
Computer Architectures

MIPS Control

Zhu Wen-Jun

Institute of Computer

Outline

- Datapath Review
 - Controller Implementation
-

Great Idea #1: Levels of Representation/Interpretation

Higher-Level Language
Program (e.g. C)

↓ *Compiler*

Assembly Language
Program (e.g. MIPS)

↓ *Assembler*

Machine Language
Program (MIPS)

```
temp = v[k];  
v[k] = v[k+1];  
v[k+1] = temp;
```

```
lw    $t0, 0($2)  
lw    $t1, 4($2)  
sw    $t1, 0($2)  
sw    $t0, 4($2)
```


```
0000 1001 1100 0110 1010 1111 0101 1000  
1010 1111 0101 1000 0000 1001 1100 0110  
1100 0110 1010 1111 0101 1000 0000 1001  
0101 1000 0000 1001 1100 0110 1010 1111
```

↓ *Machine
Interpretation*


Hardware Architecture Description
(e.g. block diagrams)

↓ *Architecture
Implementation*

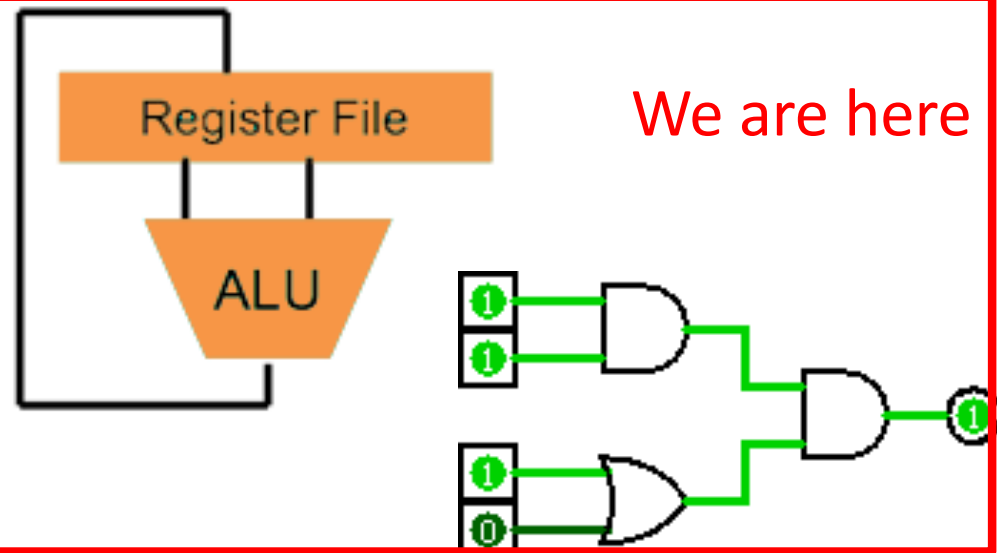Logic Circuit Description
(Circuit Schematic Diagrams)



Hardware Design Hierarchy

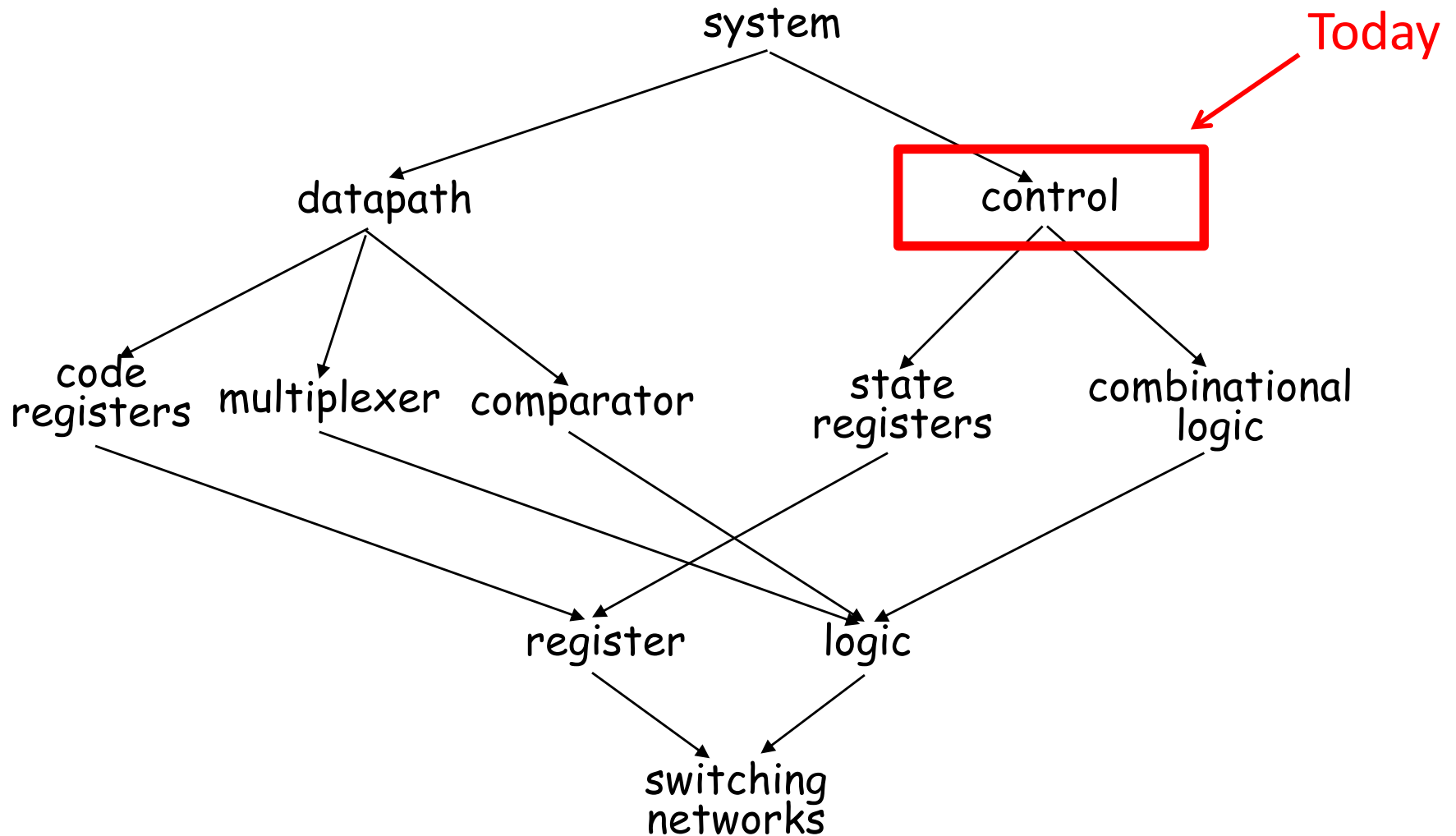


Outline

- Datapath Review
 - Controller Implementation
-

Datapath Review

- Part of the processor; the *hardware* necessary to perform *all* operations required
 - Depends on exact ISA, RTL of instructions
- Major components:
 - PC and Register File (RegFile holds registers)
 - Instruction and Data Memory
 - ALU for operations (on two operands)
 - Extender (sign/zero extend)


Five Stages of the Datapath

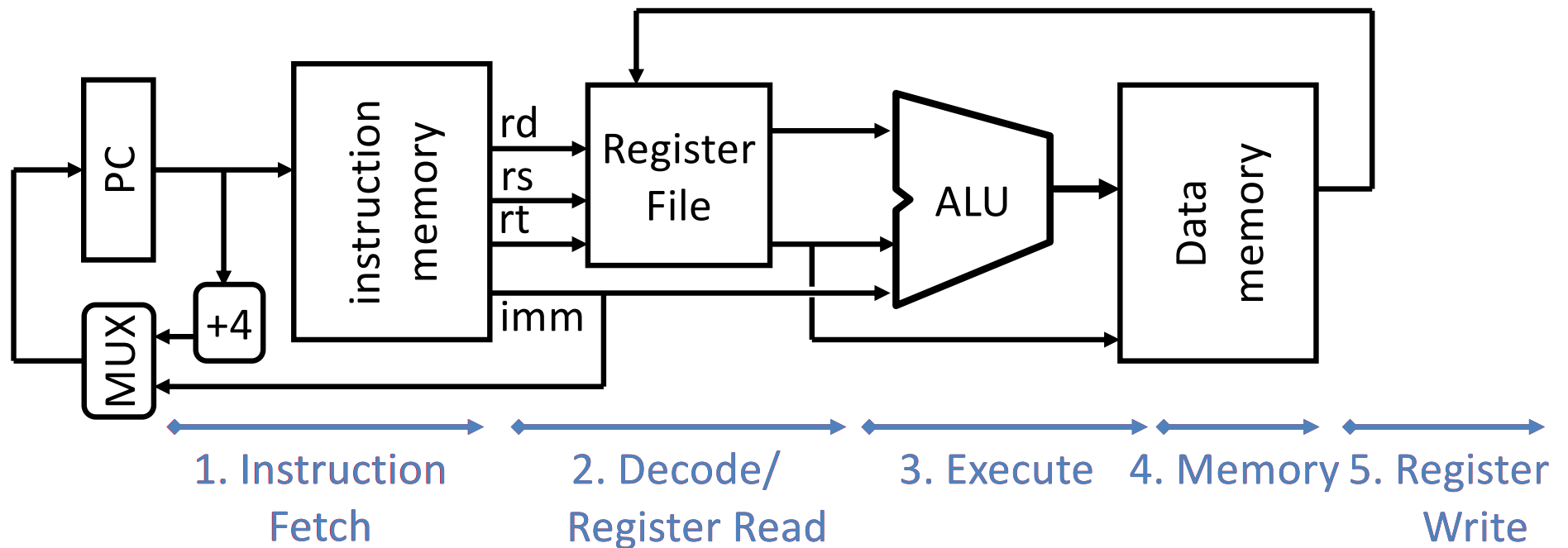

Datapath and Control


- Route parts of datapath based on ISA needs
 - Add MUXes to select from multiple inputs
 - Add *control signals* for component inputs and MUXes
- Analyze control signals
 - How wide does each one need to be?
 - For each instruction, assign appropriate value for correct routing

MIPS-lite Instruction Fetch

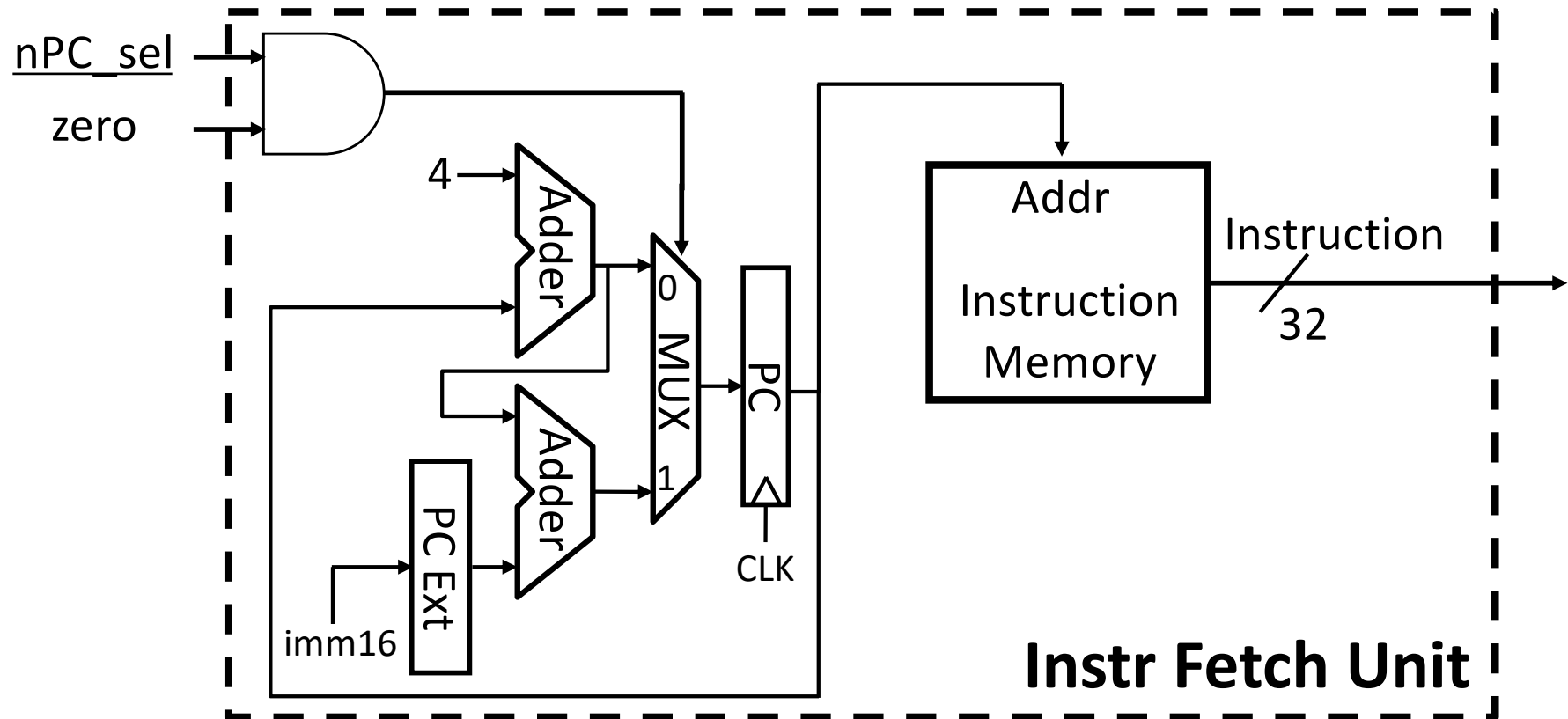

MIPS-lite Datapath Control Signals

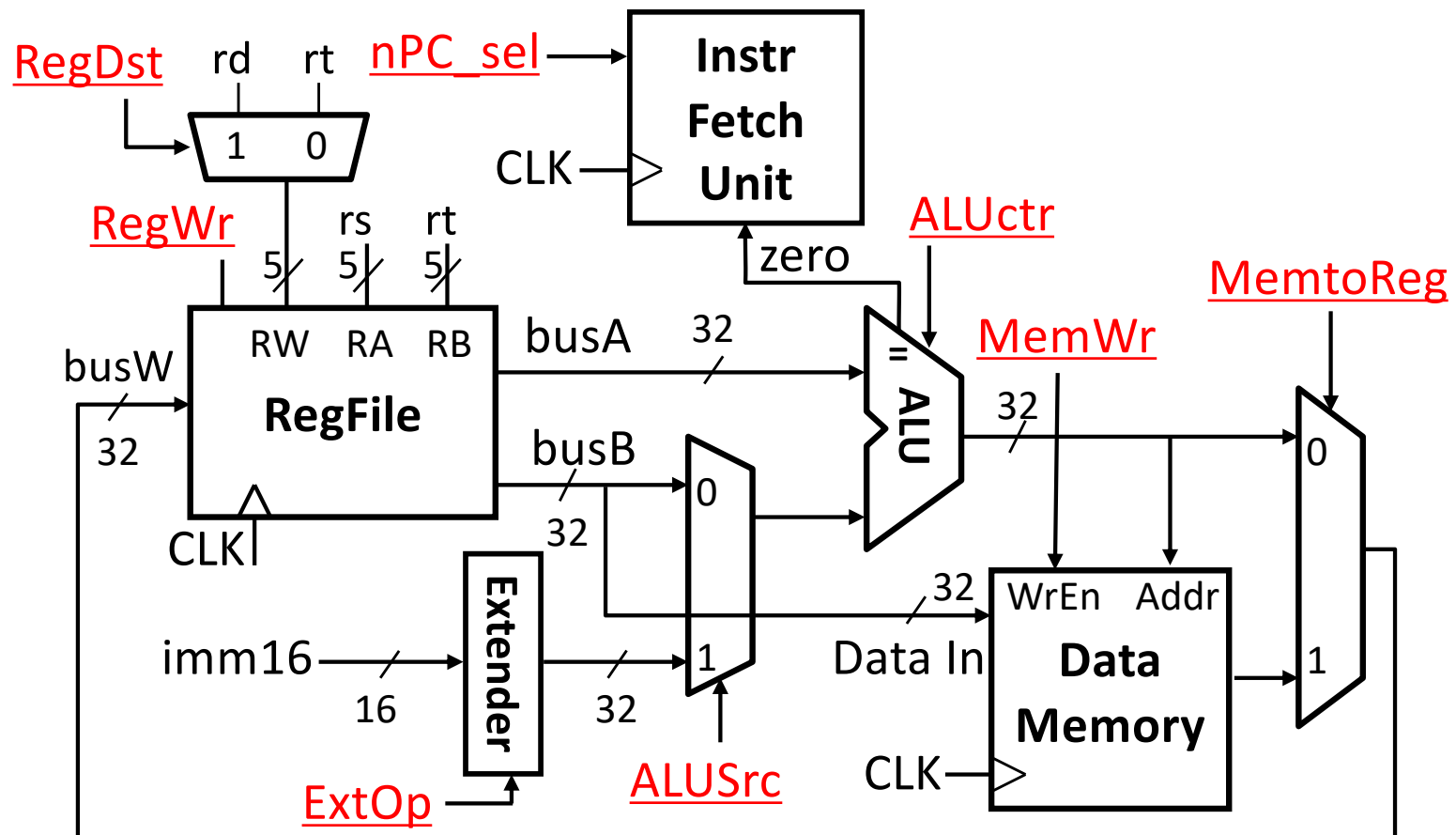- **ExtOp:** 0 \rightarrow "zero"; 1 \rightarrow "sign"
- **ALUsrc:** 0 \rightarrow busB; 1 \rightarrow imm16
- **ALUctr:** "ADD", "SUB", "OR"
- **nPC_sel:** 0 \rightarrow +4; 1 \rightarrow branch
- **MemWr:** 1 \rightarrow write memory
- **MemtoReg:** 0 \rightarrow ALU; 1 \rightarrow Mem
- **RegDst:** 0 \rightarrow "rt"; 1 \rightarrow "rd"
- **RegWr:** 1 \rightarrow write register



Outline

- Datapath Review
 - Controller Implementation
-

Processor Design Process

- Five steps to design a processor:

1. Analyze instruction set → datapath requirements

2. Select set of datapath components & establish clock methodology


3. Assemble datapath meeting the requirements

4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer


5. Assemble the control logic

- Formulate Logic Equations
- Design Circuits

Now

 

Purpose of Control

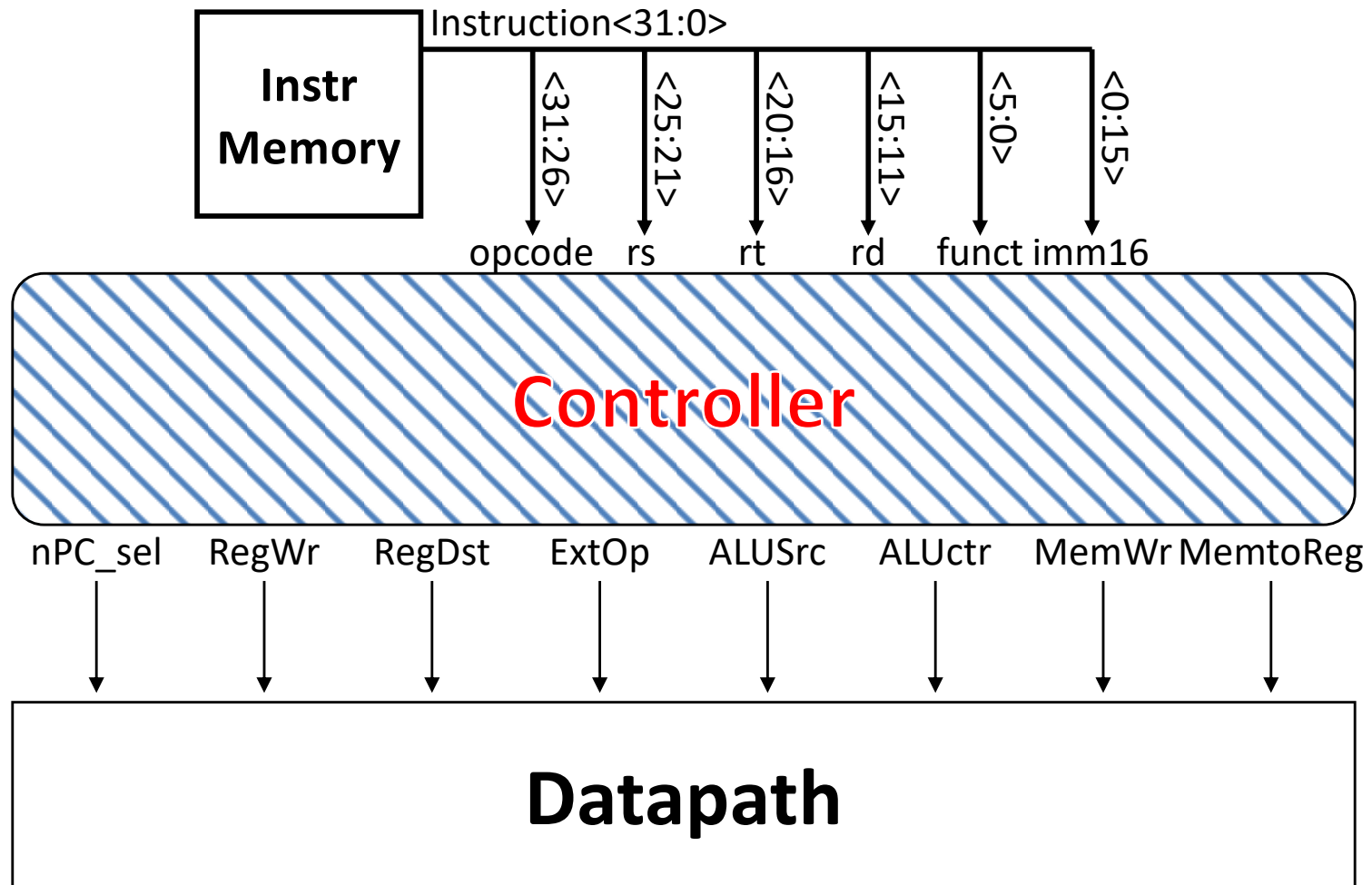

MIPS-lite Instruction RTL

Instr Register Transfer Language

addu $R[rd] \leftarrow R[rs] + R[rt]; \quad PC \leftarrow PC + 4$

subu $R[rd] \leftarrow R[rs] - R[rt]; \quad PC \leftarrow PC + 4$

ori $R[rt] \leftarrow R[rs] + \text{zero_ext}(\text{imm16}); \quad PC \leftarrow PC + 4$

lw $R[rt] \leftarrow \text{MEM}[R[rs] + \text{sign_ext}(\text{imm16})];$
 $PC \leftarrow PC + 4$

sw $\text{MEM}[R[rs] + \text{sign_ext}(\text{imm16})] \leftarrow R[rs];$
 $PC \leftarrow PC + 4$

beq $\text{if } (R[rs] == R[rt])$
 $\text{then } PC \leftarrow PC + 4 + [\text{sign_ext}(\text{imm16}) || 00]$
 $\text{else } PC \leftarrow PC + 4$

MIPS-lite Control Signals (1/2)

Instr	Control Signals
addu	ALUsrc=RegB, ALUctr="ADD", RegDst=rd, RegWr, nPC_sel="+4"
subu	ALUsrc=RegB, ALUctr="SUB", RegDst=rd, RegWr, nPC_sel="+4"
ori	ALUsrc=Imm, ALUctr="OR", RegDst=rt, RegWr, ExtOp="Zero", nPC_sel="+4"
lw	ALUsrc=Imm, ALUctr="ADD", RegDst=rt, RegWr, ExtOp="Sign", MemtoReg, nPC_sel="+4"
sw	ALUsrc=Imm, ALUctr="ADD", MemWr, ExtOp="Sign", nPC_sel="+4"
beq	ALUsrc=RegB, ALUctr="SUB", nPC_sel="Br"

MIPS-lite Control Signals (2/2)

See MIPS Green Sheet → **func**
→ **op**

	10 0000	10 0010	n/a			
	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100
	add	sub	ori	lw	sw	beq
RegDst	1	1	0	0	X	X
ALUSrc	0	0	1	1	1	0
MemtoReg	0	0	0	1	X	X
RegWrite	1	1	1	1	0	0
MemWrite	0	0	0	0	1	0
nPC_sel	0	0	0	0	0	1
ExtOp	X	X	0	1	1	X
ALUctr<2:0>	Add	Subtract	Or	Add	Add	Subtract

Control Signals

All Supported Instructions

- Now how do we implement this table with CL?

Generating Boolean Expressions

- **Idea #1:** Treat instruction names as Boolean variables!
 - `opcode` and `funct` bits are available to us
 - Use gates to generate signals that are 1 when it is a particular instruction and 0 otherwise

- **Examples:**

`beq = op[5]' · op[4]' · op[3]' · op[2] · op[1]' · op[0]'`

`Rtype = op[5]' · op[4]' · op[3]' · op[2]' · op[1]' · op[0]'`

`add = Rtype · funct[5] · funct[4]' · funct[3]'`
`· funct[2]' · funct[1]' · funct[0]'`


Generating Boolean Expressions

- **Idea #2:** Use instruction variables to generate control signals
 - Make each control signal the combination of all instructions that need that signal to be a 1
- **Examples:**
 - `MemWrite = sw`
 - `RegWrite = add + sub + ori + lw`
- **What about don't cares (X's)?**
 - Want simpler expressions; set to 0!


} Read
from row
of table

Controller Implementation

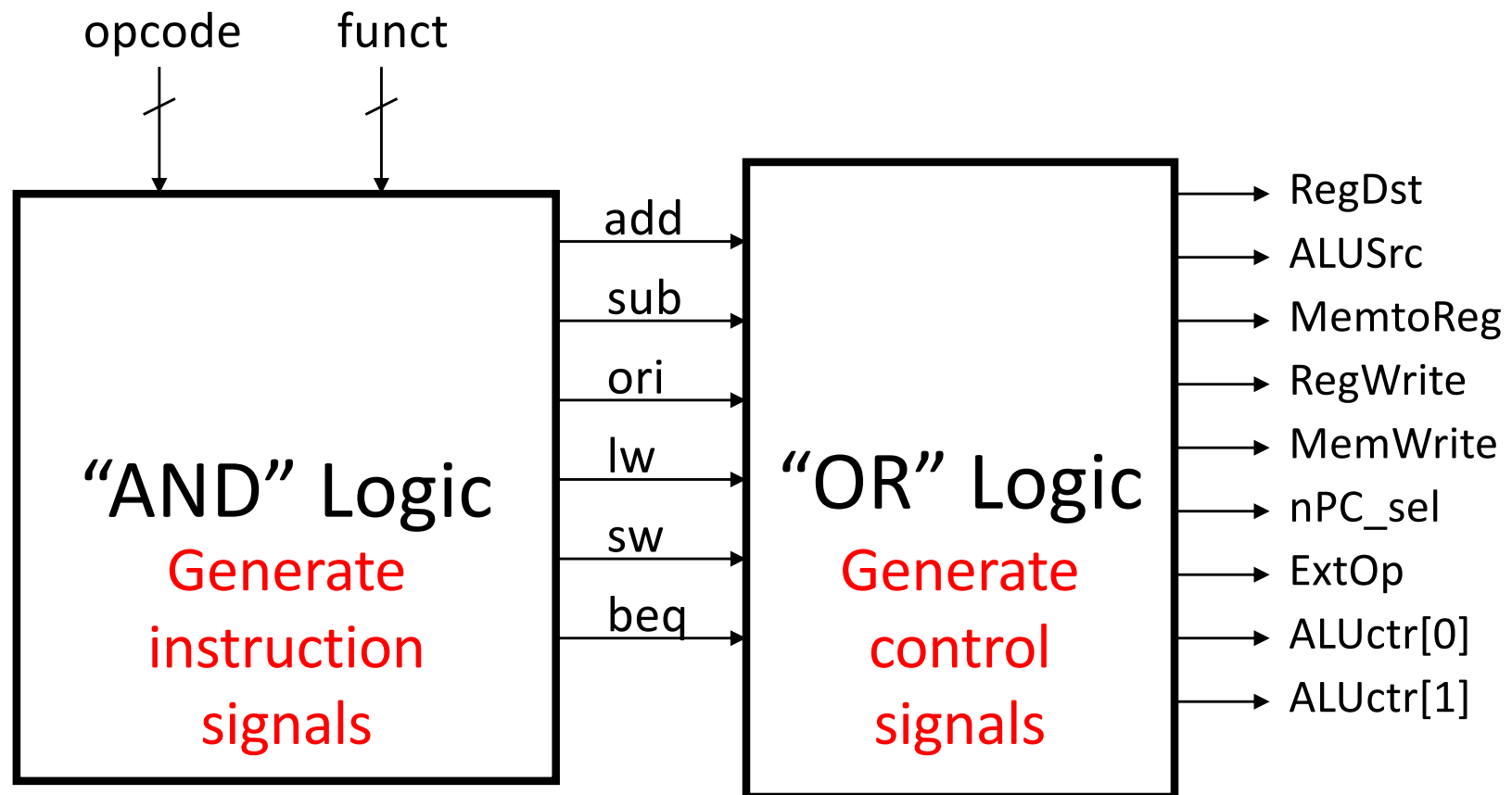
- Use these two ideas to design controller:



AND Control Logic in Logisim

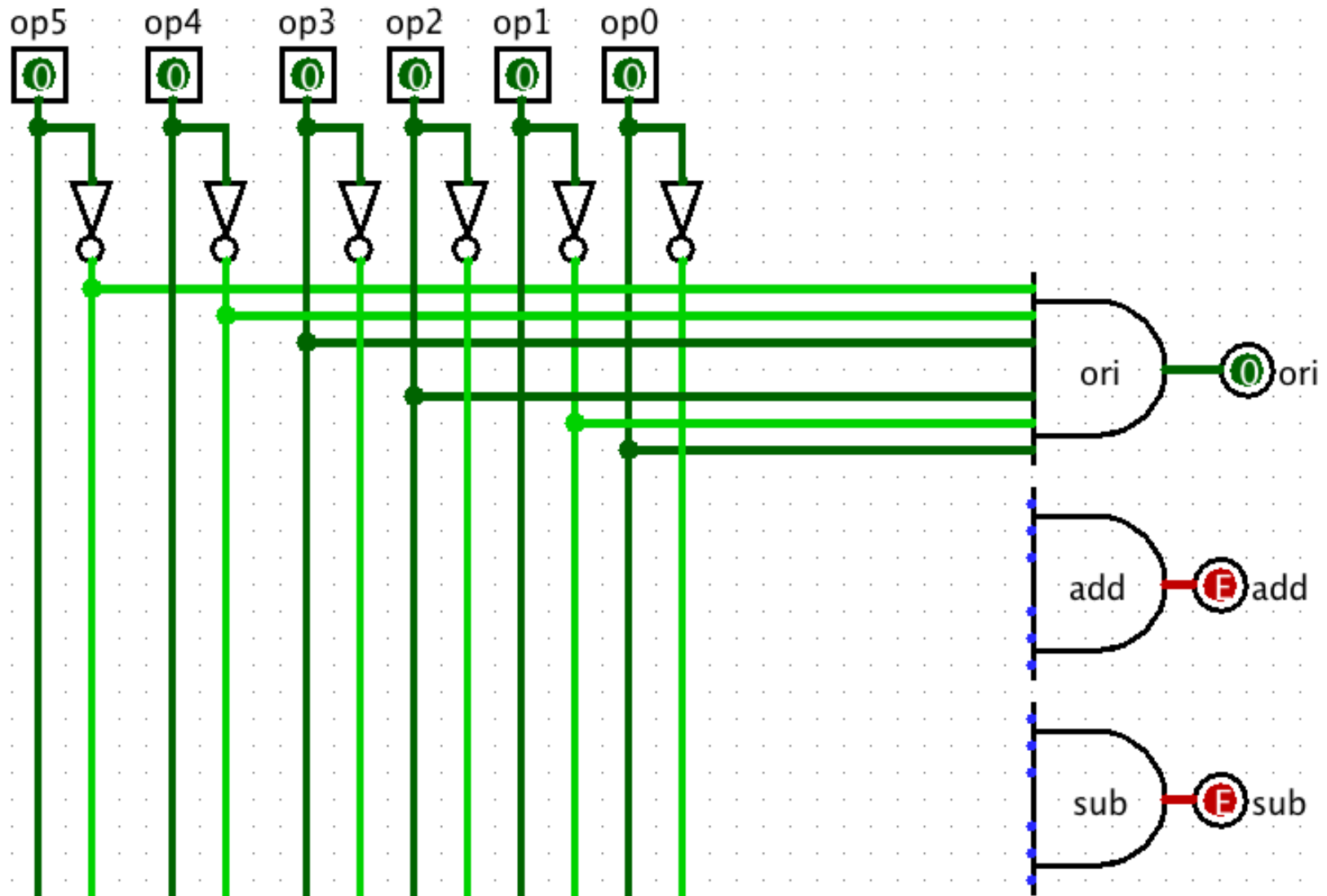

OR Control Logic in Logisim

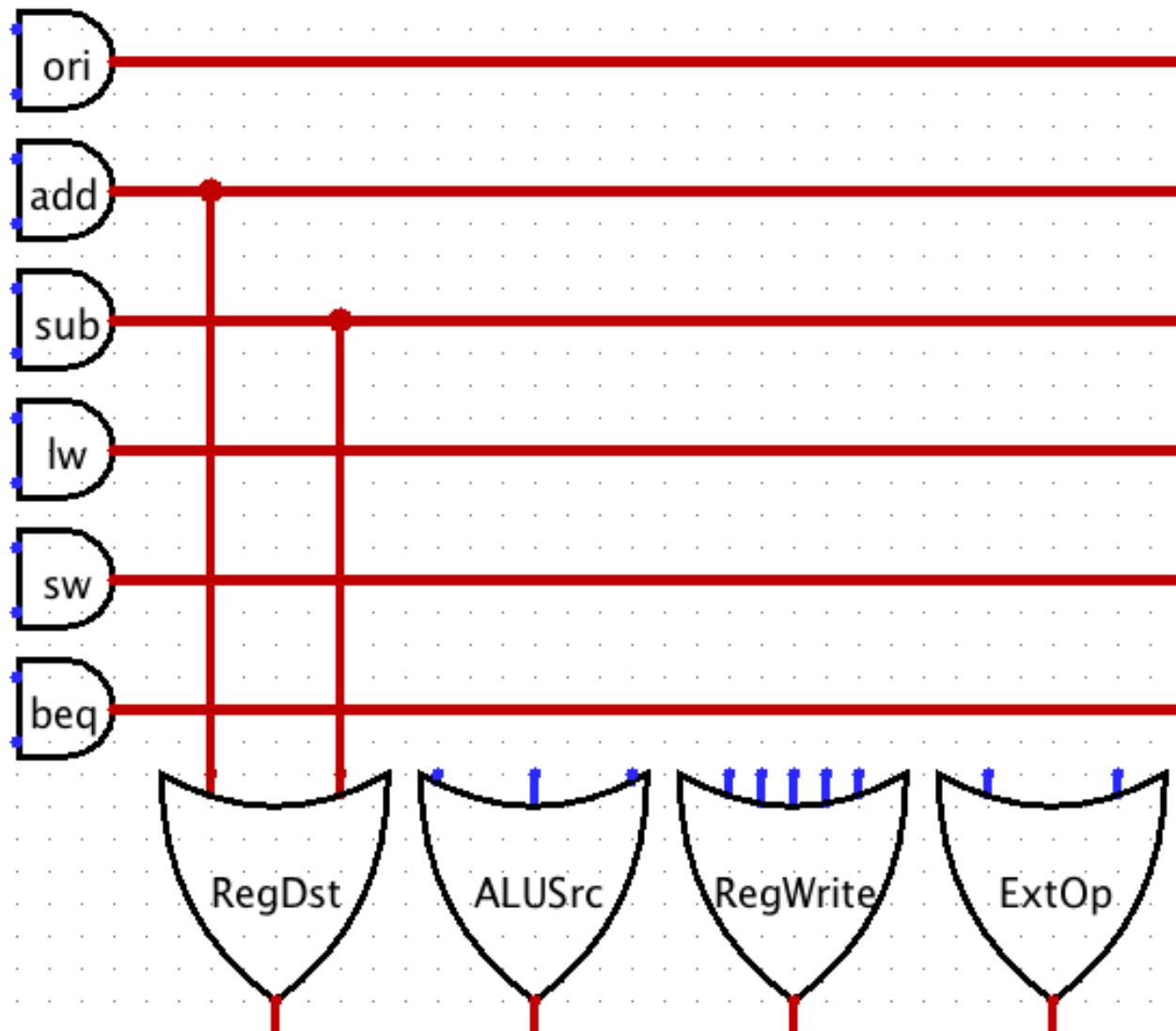

Great Idea #1: Levels of Representation/Interpretation

