

EEEN3006J

Wireless Systems

Dr. Declan Delaney

(declan.delaney@ucd.ie)



Beijing Dublin International College


Purpose of the lecture

- In this lecture, we will discuss how to make local oscillators of certain frequency.
- Oscillators are non-linear circuits that take in DC power and output a particular frequency.
- Used in transmitters as:
 - carrier signal into modulator
 - oscillator to drive mixer for up-conversion
- Used in receivers as:
 - local oscillator for mixer for down-conversion
 - local oscillator for demodulation



Purpose of this lecture

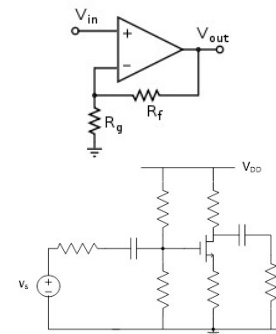
- We usually make them using an amplifier with feedback.
 - The amplifier can be made using
 - Op-amps (Only at lower frequencies), or
 - Transistors
- We usually make them using feedback made up of passive RC or LC circuits.
- Later in the lecture, we will see how to take a very stable low-frequency oscillator and make a tuneable high-frequency oscillator from it.



What makes a good oscillator?




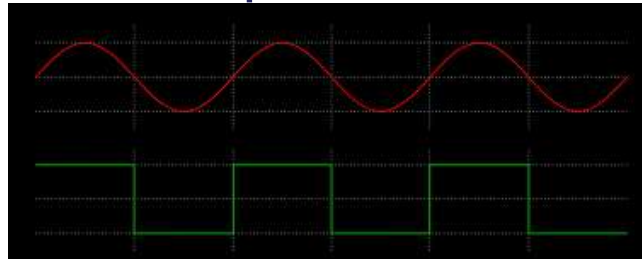- A periodic signal
 - often sinusoidal signal
 - sometimes a square-wave.



- Frequency may be
 - Fixed value, or
 - controlled by voltage or temperature.
 - VCO = voltage controlled oscillator.

Need: Frequency Stability

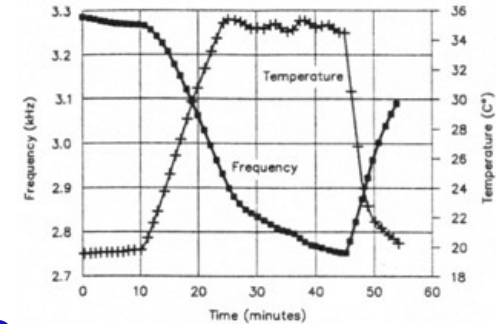


Temperature drift in a 7-MHz variable-frequency oscillator. $\sim 10^4$ ppm/°C

- Average frequency is accurate
 - over time, and
 - over a reasonable temperature range
- The permitted error \propto signal bandwidth
 - Easy case: baseband signal, large bandwidth.
 - Difficult case: narrow-band, high-frequency.
- We measure:
 - Error, in parts per million (ppm) or parts per billion (ppb).
 - Variation with temperature; ppm/°C or Hz/°C.
 - Ageing; ppm/year.



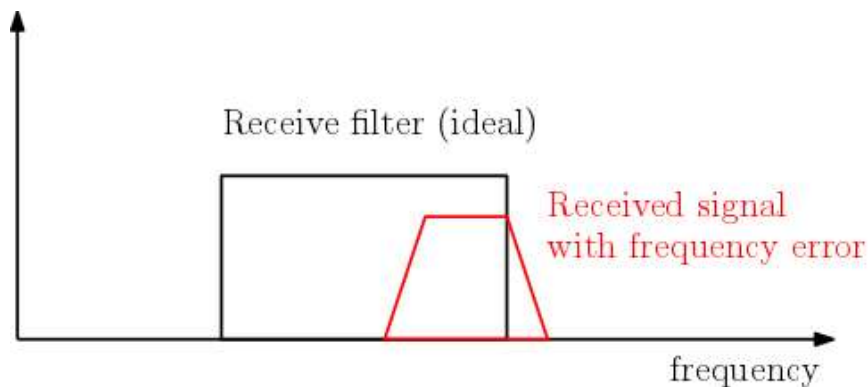- The transmitter needs to transmit at the correct frequency
 - transmit where receiver is expecting signal
 - avoid interference with neighbours
- The receiver needs to shift the frequency of the input signal by the correct amount
 - otherwise wanted signal will not pass through filter.




Datasheet example

MOFH and MOFZ Series / 14 Pin DIP OCXO



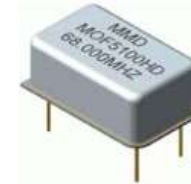- Oven Controlled Oscillator
- 1.0 MHz to 150.0 MHz Available
- 14-pin DIP Package
- -40°C to 85°C Available
- ±50ppb to ±500ppb



PART NUMBERING GUIDE:

MOF H 5 S 100 B - Frequency

Output Type
H = HCMOS
Z = Sinewave

Supply Voltage
3 = 3.3 Volt
5 = 5 Volt
12 = 12 Volt

Crystal Cut*
Blank = AT Cut
S = SC Cut

Operating Temperature
A = 0°C to 50°C
B = -10°C to 60°C
C = -20°C to 70°C
D = -30°C to 70°C
E = -30°C to 80°C
F = -40°C to 85°C
G = 0°C to 70°C

Frequency Stability
050 = ±50ppb
100 = ±100ppb
250 = ±250ppb
500 = ±500ppb

*Specific Stabilities/ Temperatures requires an SC Cut Crystal


ELECTRICAL SPECIFICATIONS:

Frequency Range		1.0 MHz to 150.0MHz		
Frequency Stability		±50ppb to ±500ppb		
Operating Temperature		-40°C to 85°C max*		
* All stabilities not available, please consult MMD for availability.				
Storage Temperature		-40°C to 95°C		
Output	Sinewave	±3 dBm		50Ω
	HCMOS	10% Vdd max 90% Vdd min		30pF
Supply Voltage (Vdd)		3.3V	5V	12V
Supply Current	typ	220mA	200mA	80mA
	max	550mA	400mA	150mA
Warm-up Time		3min. @ 25°C		
Input Impedance		100K Ohms typical		
Crystal		AT or SC Cut options		
Phase Noise @ 10MHZ		SC		AT
10 Hz Offset		-100dBc		-92dBc
100 Hz Offset		-127dBc		-118dBc
1000 Hz Offset		-140dBc		-135dBc
Voltage Control 0 to VCC		±3ppm typ		±10ppm typ
Aging (after 30 days)		±0.5ppm/yr.		±1.5ppm/yr.

MECHANICAL DETAILS:



Need: Spectral Purity

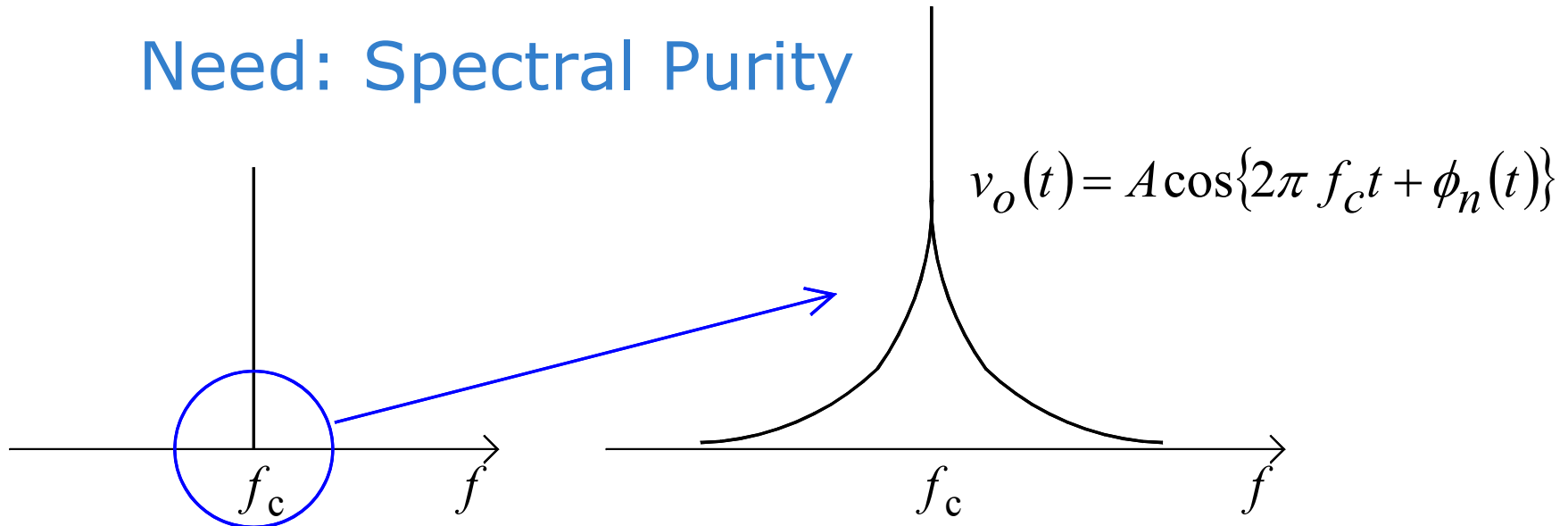

- One line in frequency spectrum
 - no harmonics, no other spurious outputs
- Phase noise = random phase modulation
 - due to random noise in circuit (flicker noise)
 - affects amplitude and phase, but oscillator amplitude control reduces amplitude changes
 - specify power spectral density at some offset
 - e.g. -95 dBc/Hz at 100 kHz
 - dBc = dB relative to carrier (wanted output)

Often Want Frequency Agility


- Frequency adjustable
 - transmitter works over some range of freq.
 - receiver must receive over some range of freq.
- Specify frequency range, step size
 - step size corresponds to channel spacing
- Speed of adjustment
 - frequency-hopping systems - rapid changes
 - generator settles on new frequency quickly
- Conflict with frequency stability
 - oscillator designed for stability usually not adjustable, certainly not quickly



We make oscillators using feedback

- Oscillators: nonlinear circuits convert DC power to AC.

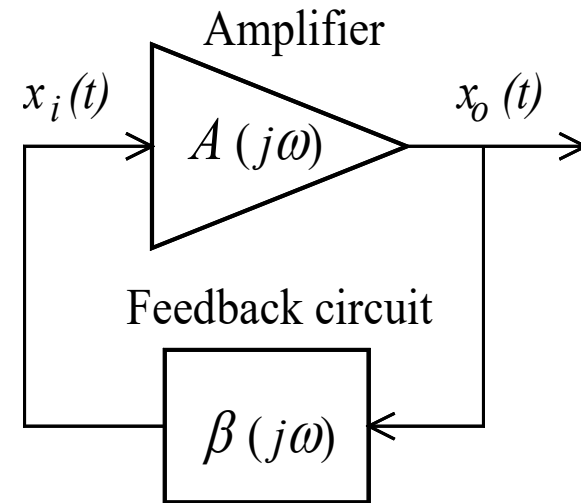- Ideally a sinusoid (simpler to design around.)



- Basic idea: amplifier with positive feedback
 - Barkhausen criterion: $A(j\omega) \cdot \beta(j\omega) = 1 + j0$ at some frequency ω .

$$x_o = A x_i + A \beta x_o$$


$$x_o = \frac{A}{1 - A \beta} x_i$$



Barkhausen criterion
makes the
denominator zero.



Basic sinusoidal oscillator

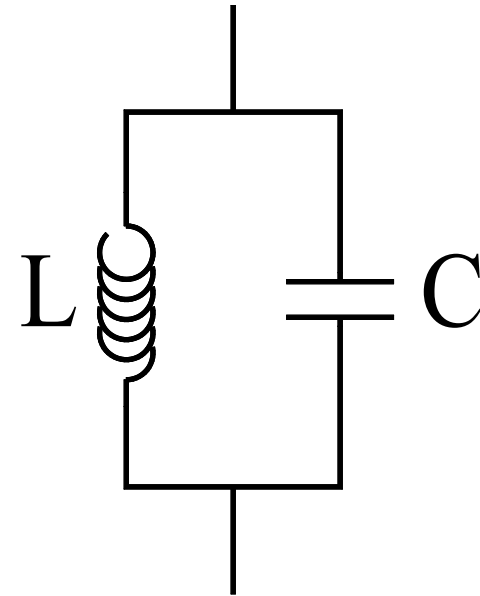- need narrow bandwidth for spectral purity
 - could use L-C resonant circuit (high Q factor)?
 - for narrower bandwidth, use mechanical resonator
- some non-linearity controls amplitude
 - usually in amplifier






Quartz Crystal Resonator

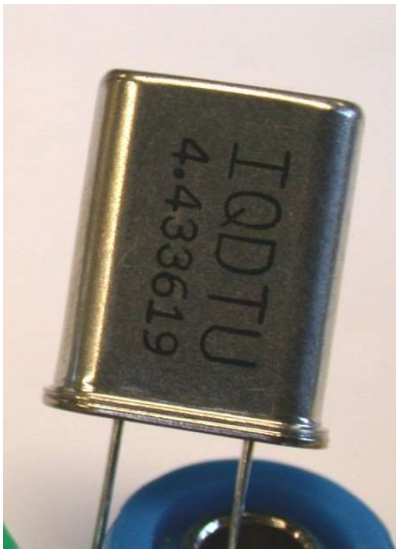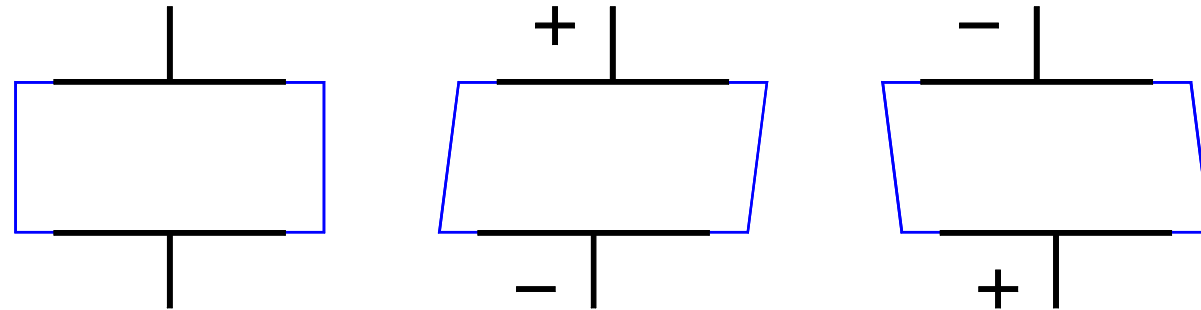

- Quartz exhibits piezo-electric effect
 - applied voltage causes shape change
 - shape change generates voltage
- Crystal acts as mechanical resonator
 - 2 electrodes, piezo-electric conversions
 - effect is electrical resonator
 - high Q-factor: 10^4 up to 10^6 possible
- Dimensions control resonant frequency
 - up to 100 MHz commonly available


Quartz Resonator

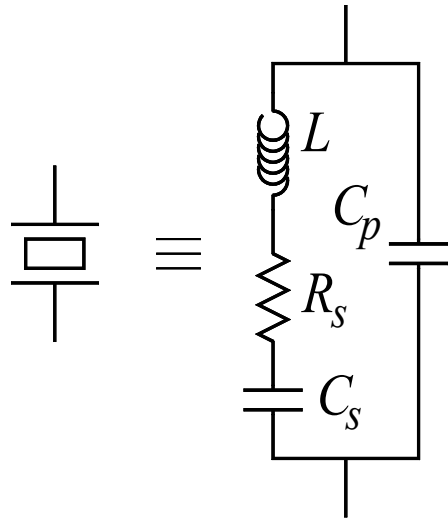

$$\omega_s = \frac{1}{\sqrt{LC_s}}$$

$$\omega_p = \frac{1}{\sqrt{LC'}}$$


$$C' = \frac{C_p C_s}{C_p + C_s}$$

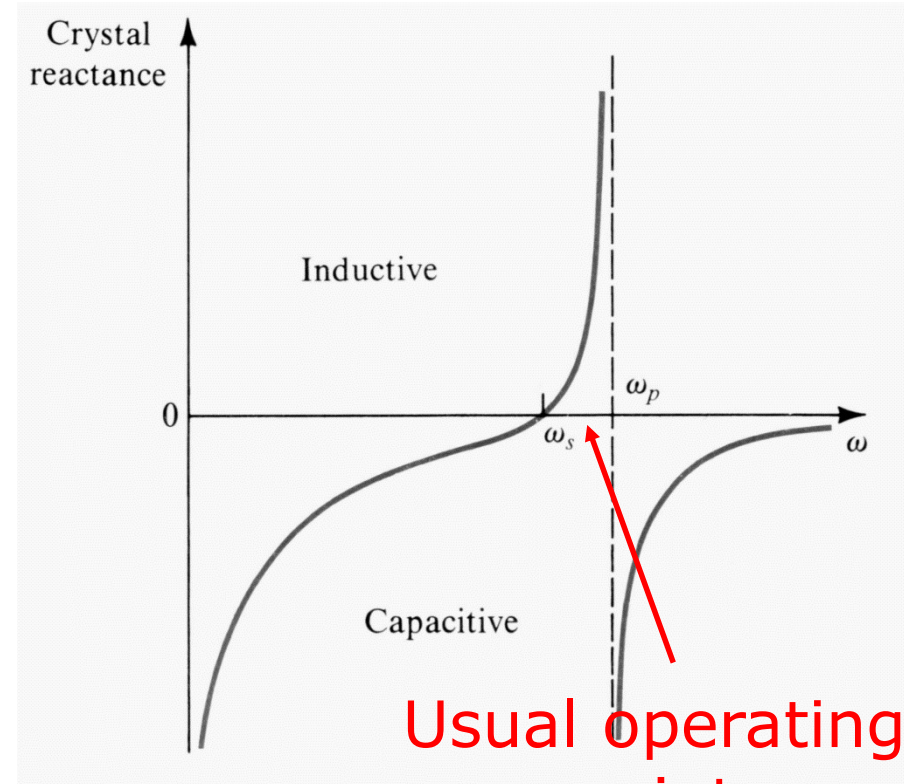

- Mechanical resonator, so model:
 - momentum as large inductance (L , H)
 - elasticity as series capacitance (C_s , fF)
 - Damping and loss as small series resistance R_s
 - also real capacitance between electrodes (pF)
- series and parallel resonances, very close



Precision Oscillator

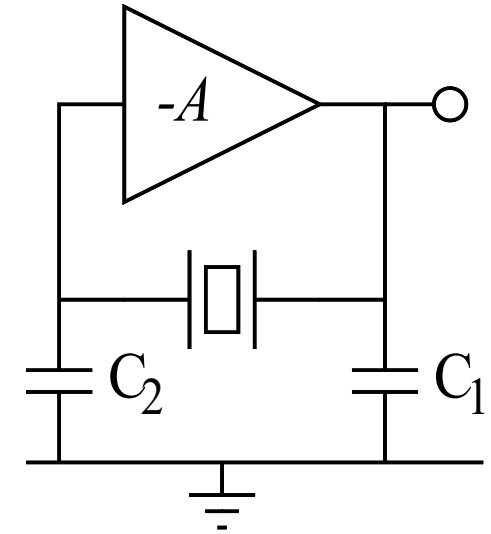


- Want precise frequency, stability, low phase noise
 - use quartz crystal resonator in feedback
 - external capacitors add to parallel capacitance...
 - allow very limited frequency adjustment - ppm
 - for higher precision, place oscillator in oven
 - temperature controlled chamber – TCXO
- Other mechanical resonators possible
 - ceramic resonators
 - similar to quartz, but not as good
 - surface acoustic wave (SAW) resonators
 - vibrations on surface, not in bulk of material




Voltage-Controlled Oscillator


$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

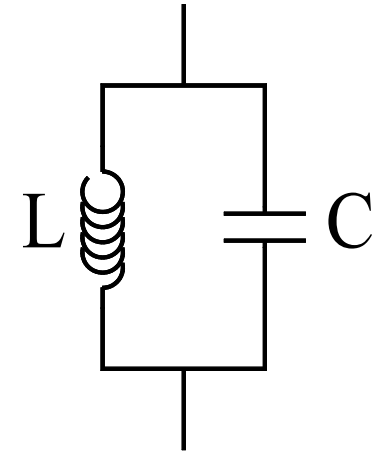

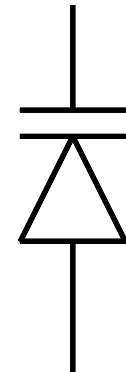- At RF, usually LC resonant circuit
 - poor precision - Q-factor $\sim 10^2$
 - (L could be transmission line stub)
- Need electrical adjustment
 - often use capacitance change in diode
 - reverse-biased by control voltage
 - special diodes are optimised for this
 - non-linear relationship
- Easy, quick to change frequency
 - limited range of adjustment
 - difficult to get precise frequency





Example: Hartley Oscillator

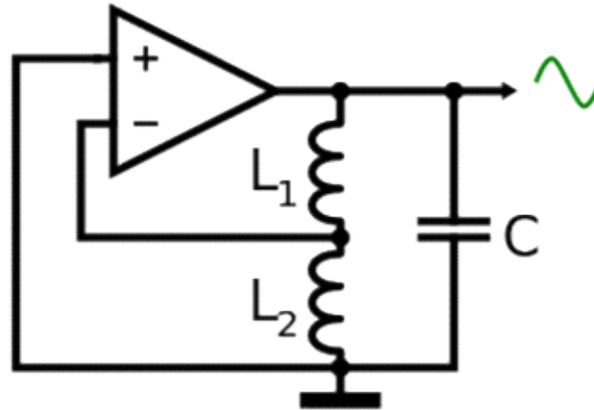

This diagram shows a variant which uses an op—amp, but transistor-based designs are also common.

- Basic oscillator uses 2 inductors & 1 capacitor
 - can also use 1 tapped inductor (mutual L)
- Modify for Voltage Controlled Oscillator – replace capacitor with varactor
 - extra capacitor (large) to isolate varactor bias
 - large inductance, “RF choke”, to isolate signal


Example: Multi-vibrator

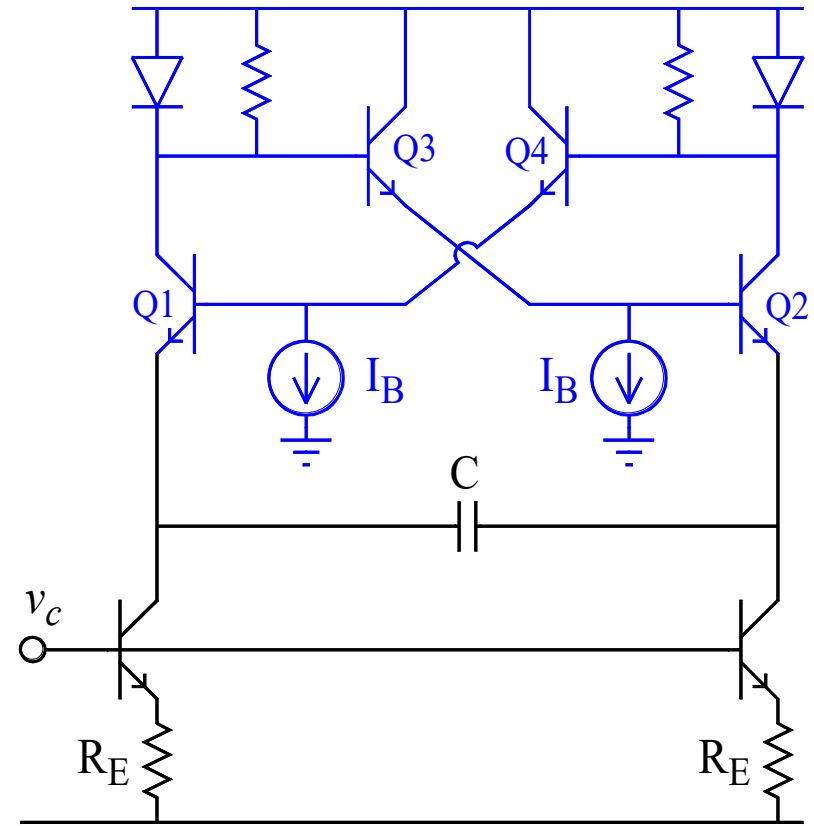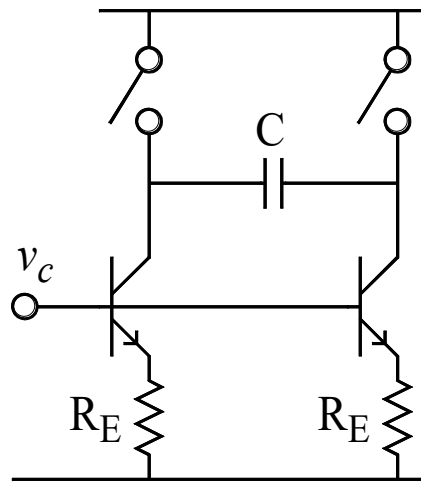

- Capacitor alternately charged & discharged
 - voltage-controlled current sources set freq.
 - switches change charging direction
- More suitable for IC implementation
 - but not at very high frequencies...




Frequency Scaling

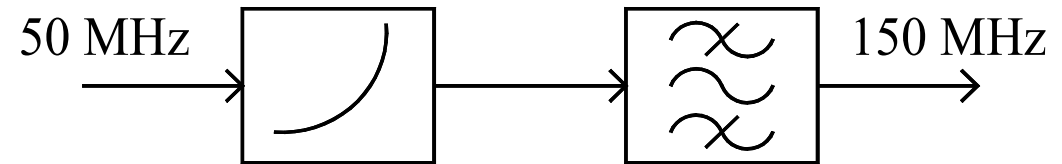

- Multiplication
 - use non-linear device to generate harmonics
 - band-pass filter to select required frequency
 - also multiplies phase noise
- Division
 - use flip-flops, counters, etc. to divide by N
 - square-wave output (could filter for sine)
 - also divides phase noise
- Addition, subtraction
 - use mixer as seen already (frequency shifting)



Phase-Locked Loop (PLL)

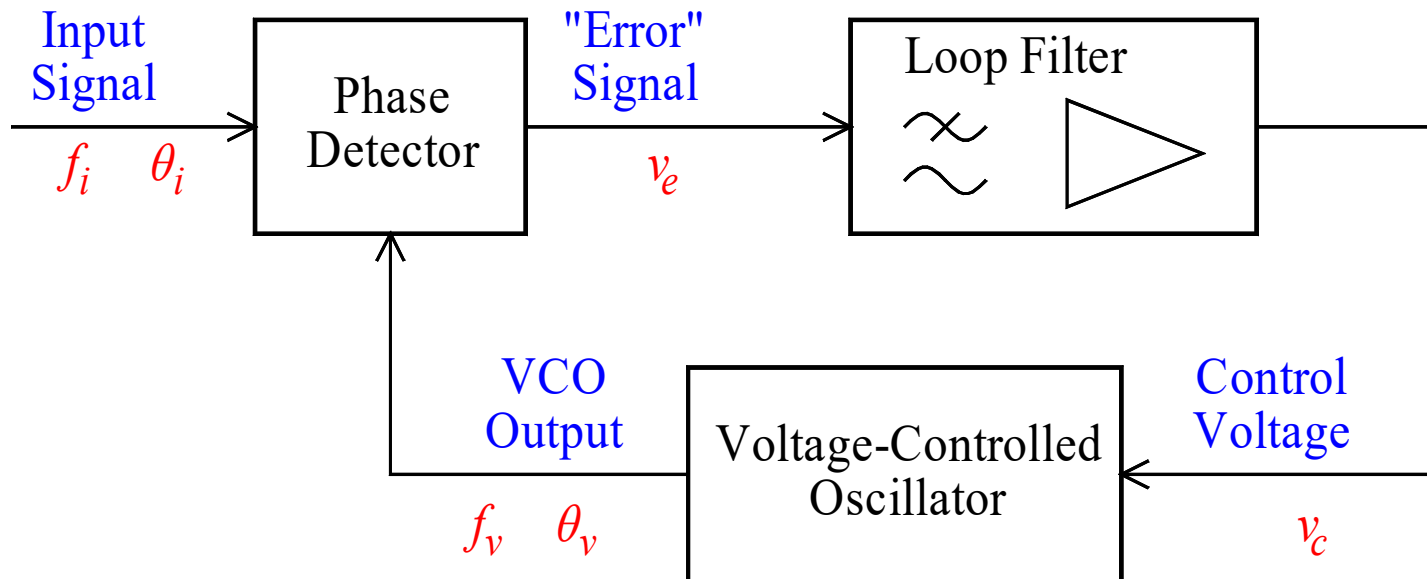

- Feedback control system
 - adjusts frequency of VCO to match input
 - phase detector measures phase difference
 - loop filter provides gain and low-pass filter
 - controls behaviour of the system





PLL Application Examples

- Noisy or modulated input
 - want VCO to follow average frequency of input
 - use loop filter with narrow bandwidth
 - in communications receiver, extract carrier frequency or clock frequency from signal...
- Frequency Modulation – demodulator
 - get VCO to follow changing input frequency
 - loop filter bandwidth must be wide enough
 - then control voltage \propto modulation...
- Frequency Synthesis
 - input from stable (e.g. crystal) oscillator
 - synchronise VCO with multiple of input freq.
 - get agility of VCO with stability of crystal...




Phase Detector Example 1

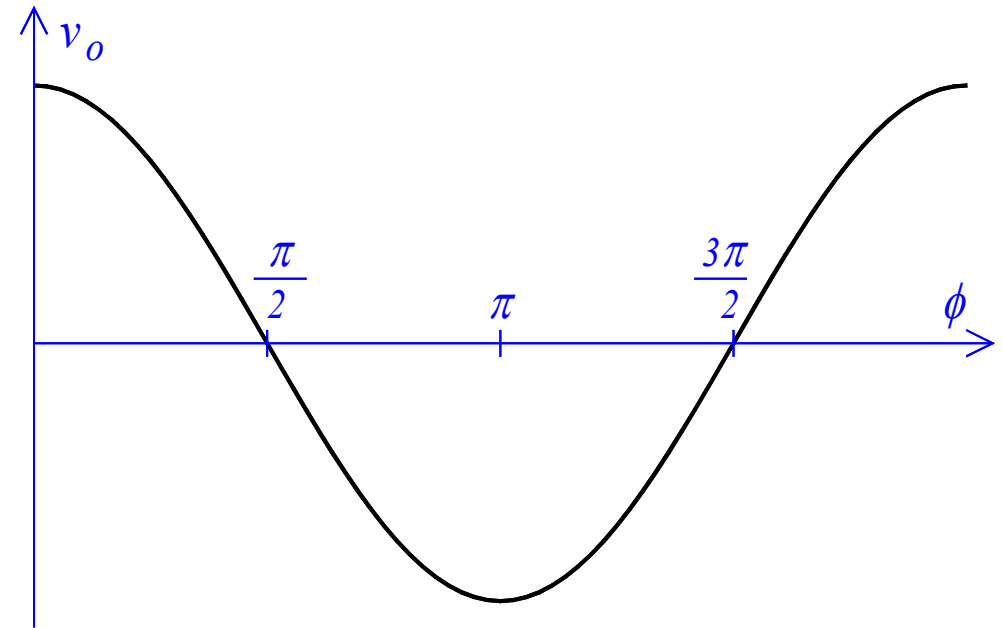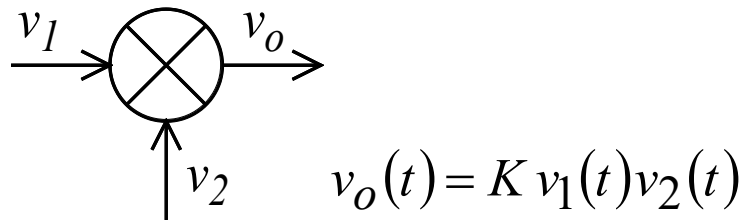

- Ideal Multiplier
 - inputs $v_1(t) = A_1 \sin(\omega_1 t)$ $v_2(t) = A_2 \sin(\omega_2 t + \phi)$
 - $v_o(t) = K \frac{A_1 A_2}{2} [\cos\{(\omega_2 - \omega_1)t + \phi\} - \cos\{(\omega_2 + \omega_1)t + \phi\}]$
 - high-frequency term removed by loop filter...
- If both frequencies equal (PLL is working properly)
 - effective $v_o(t) = K \frac{A_1 A_2}{2} [\cos(\phi)]$
- non-linear relationship phase difference \leftrightarrow output
 - \sim linear around zero output




Phase Detector Example 2

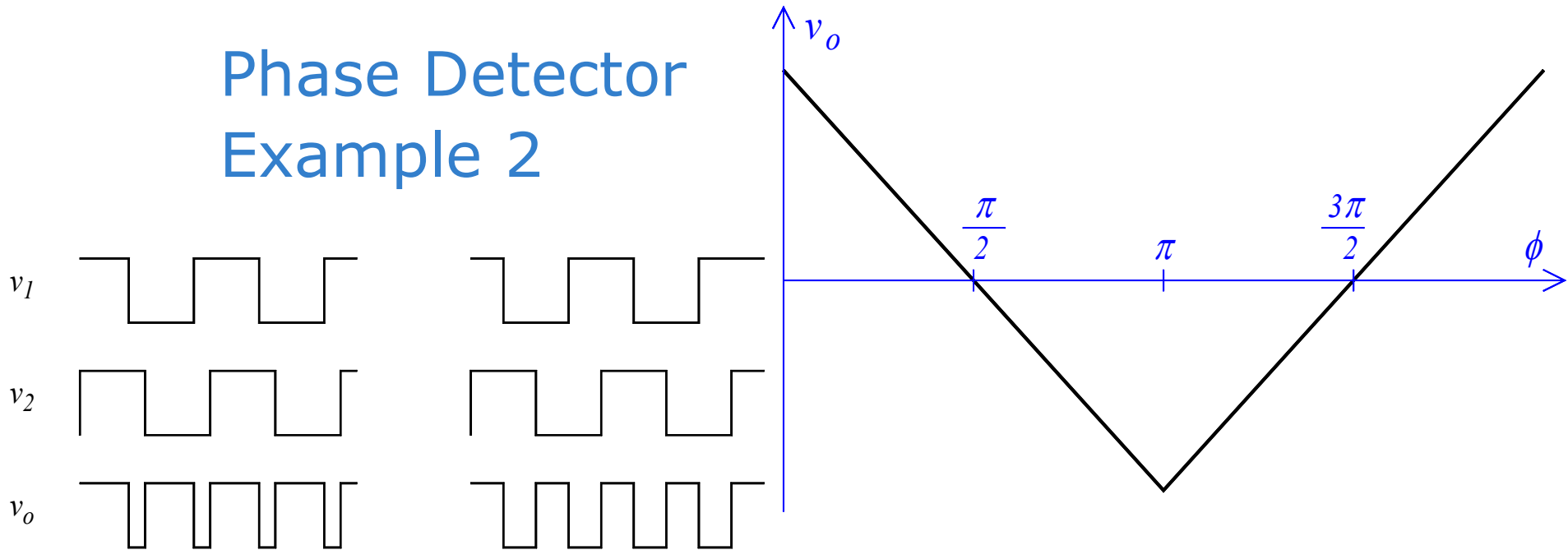

- Multiplier with square-wave signals: ± 1 V
 - exclusive-NOR gate behaves similarly
- For “phase” difference ϕ , average output

$$\overline{v_o} = \frac{K(\pi - |\phi|) - K|\phi|}{\pi} = K \left(1 - \frac{2|\phi|}{\pi} \right)$$
 assuming same freq.
 - note linear over 180° range
 - periodic in phase difference (as expected)


PLL Operation

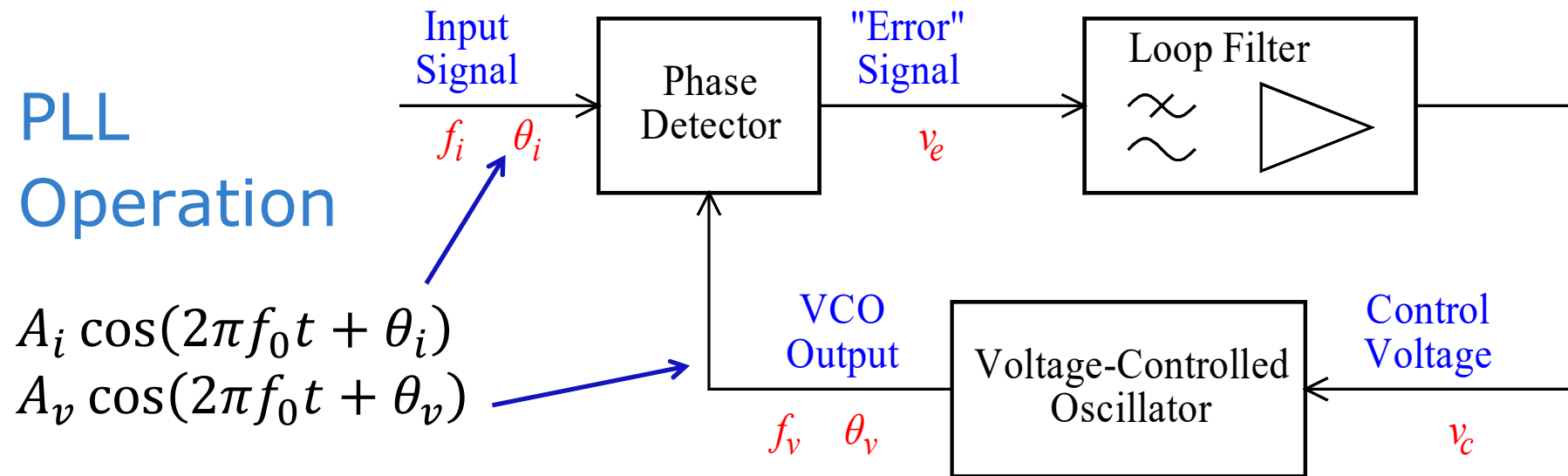

- VCO: $f_v = f_0 + k_f v_c$ $f_v = f_0 + \frac{1}{2\pi} \frac{d\theta_v}{dt}$
 - centre frequency f_0 , change proportional to v_c
 - frequency \propto rate of change of phase angle
- In normal operation, loop is "locked"
 - \Rightarrow VCO is following frequency of input signal
- If input signal at frequency f_0
 - VCO also at f_0 , so $v_c = 0$, so $v_e = 0$
 - so phase difference must be $\pm \frac{\pi}{2}$




Stable Operation?

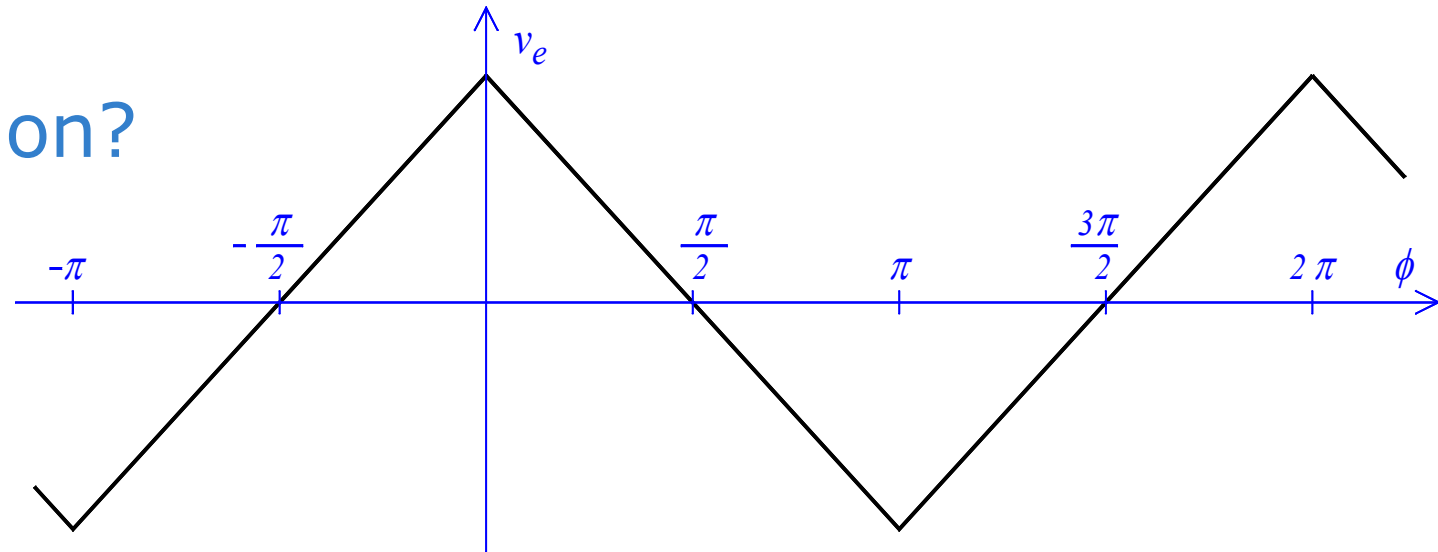

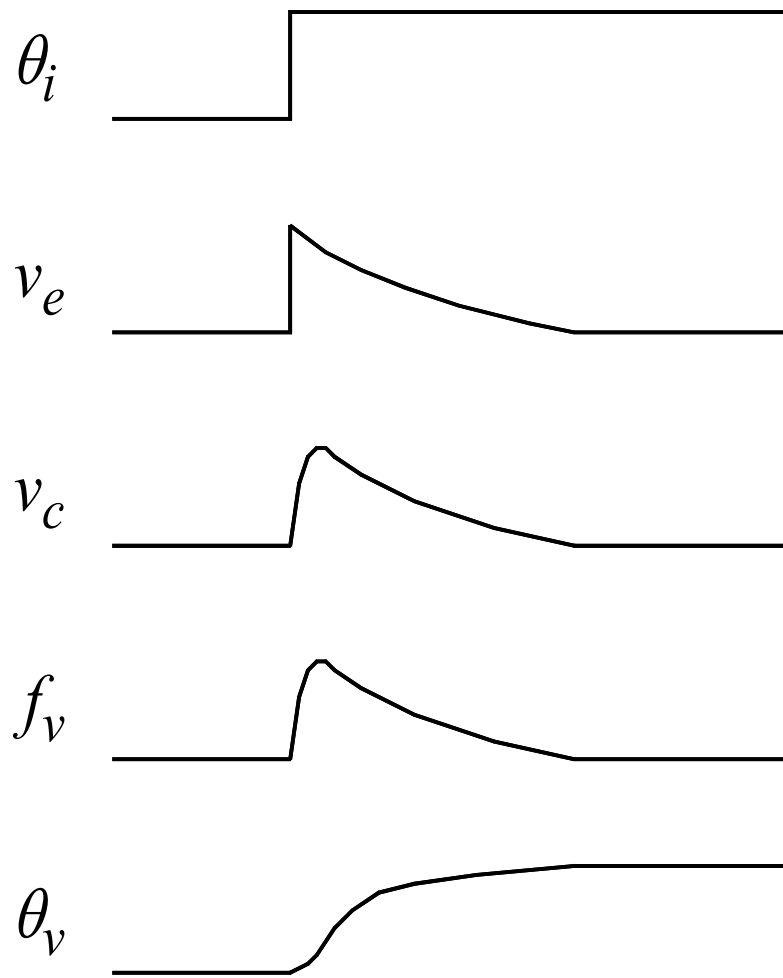- Define phase difference $\phi = \theta_i - \theta_v$
- Suppose relative phase of input advances
 - ϕ becomes larger – moving to right on graph
 - what happens to error voltage?
 - what happens to VCO control voltage?
 - what happens to VCO frequency?
 - what happens to VCO phase?
- Which operating point is stable?






$$\theta_v = \theta_0 + 2\pi \int_0^t f_v dt$$




Response to Phase Change

- Step change in θ_i
- \Rightarrow step in v_e
- $\Rightarrow v_c$ starts to rise
 - low-pass loop filter...
- so f_v follows – VCO
- so phase advances
 - \Rightarrow phase error falls...
- Settles at $v_c = 0$ again
- transient is example
 - depends on loop & filter parameters

Phase Change Example

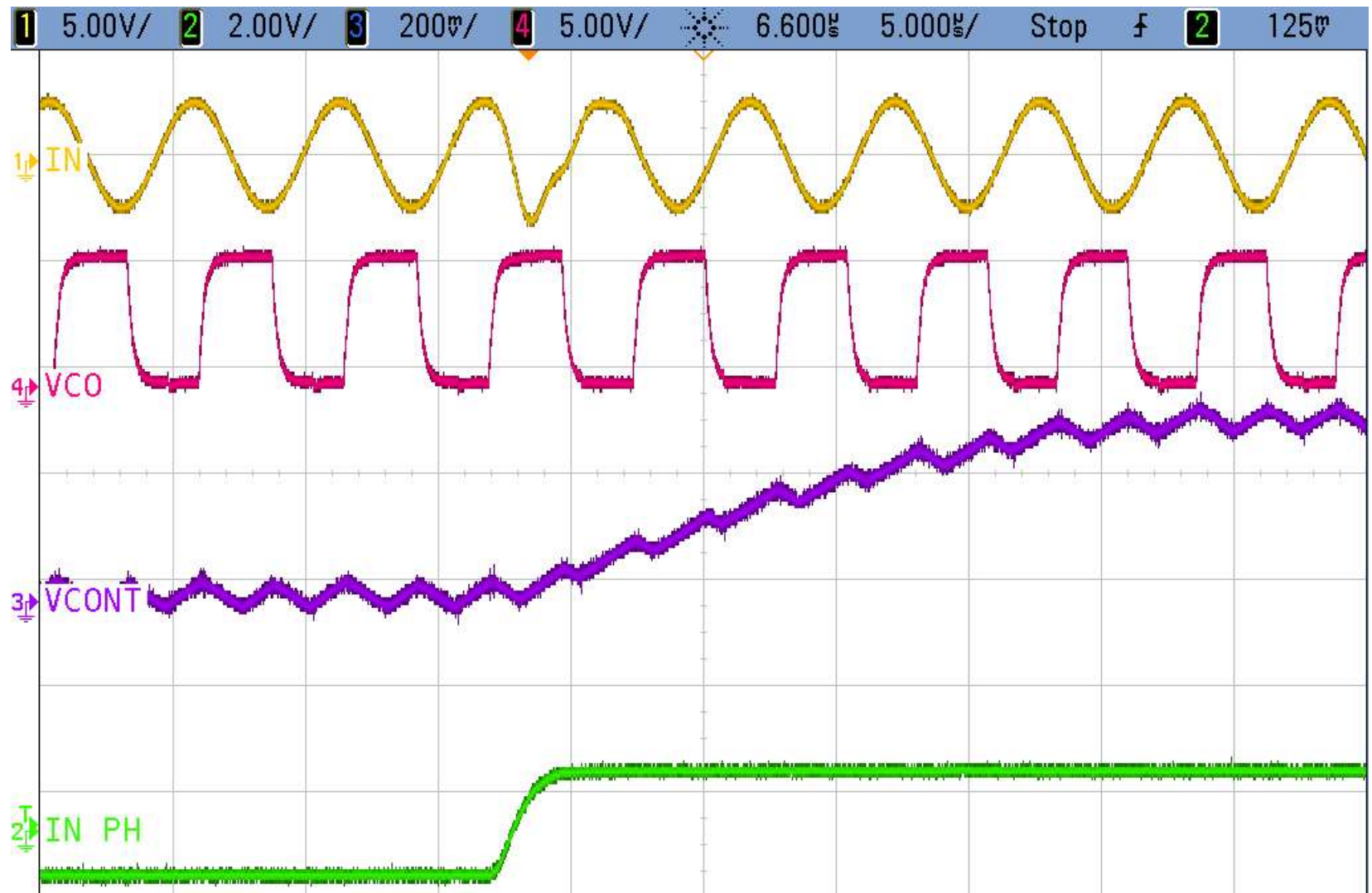

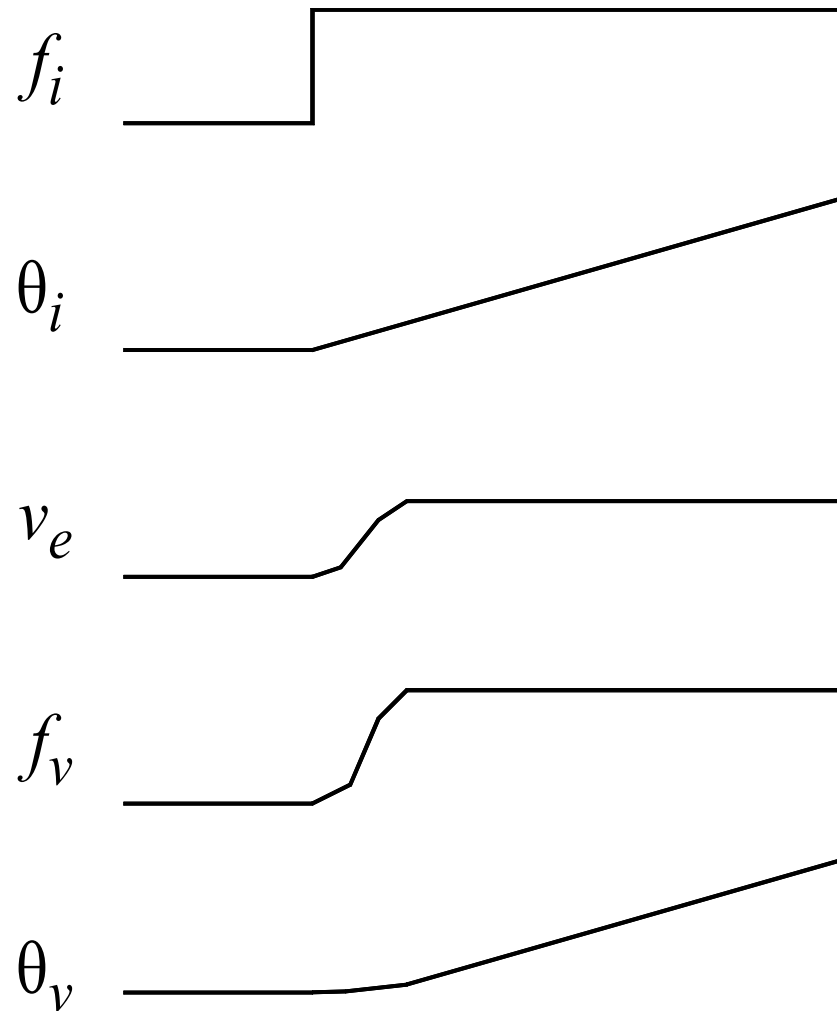


Response to Frequency Change

- Step change in $f_i \rightarrow f_0 + \Delta f$
 - so θ_i starts to advance
 - v_e increases
 - f_v follows
 - so θ_v advances also
- Settles with $v_c \neq 0$
 - needed to get higher f_v
 - so phase error needed...
- Transient is example



Frequency Change Example

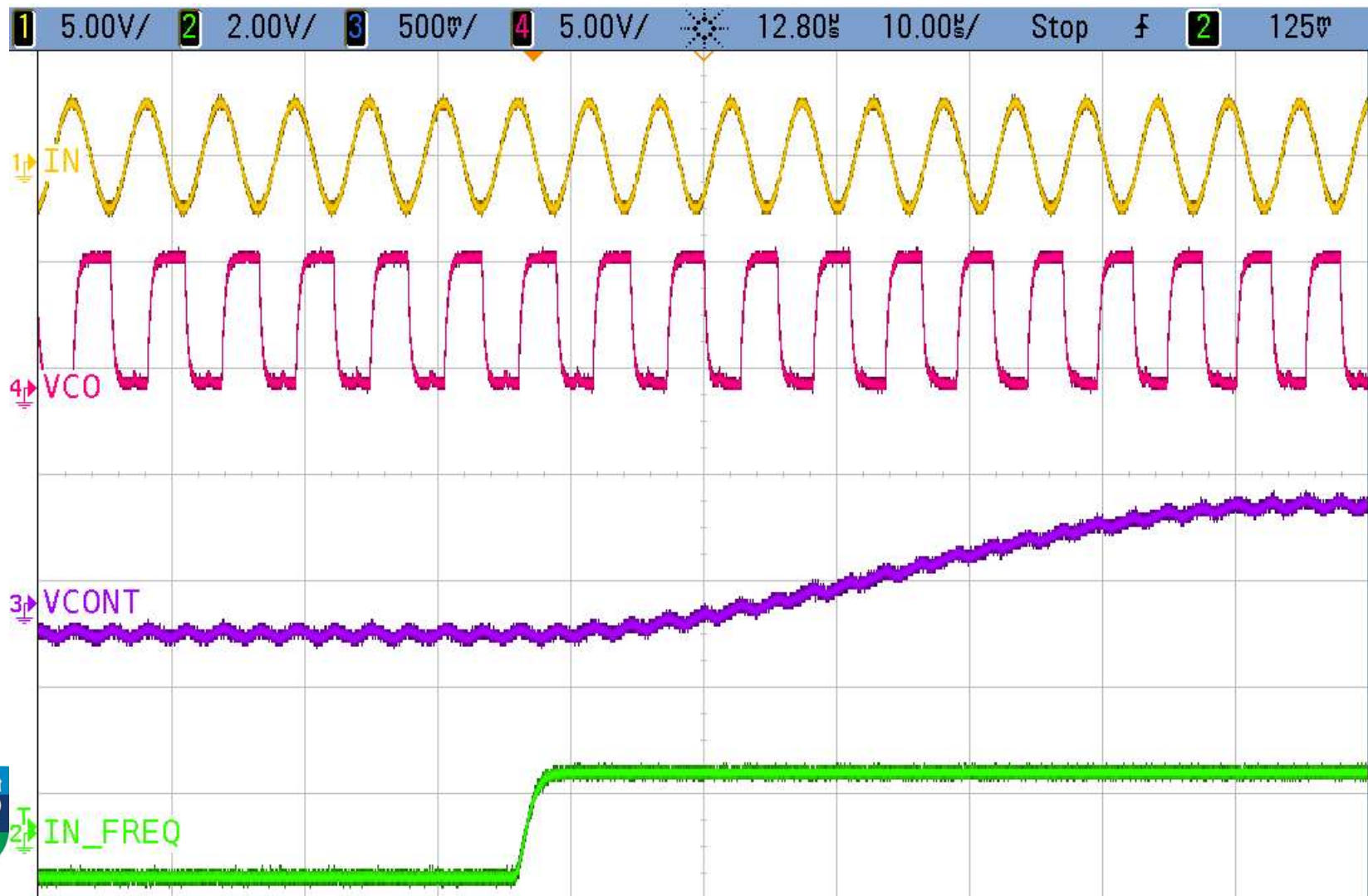

Lock Range

- We define the lock range of PLL as:
 - range of input frequency over which loop can remain locked.
- What determines the lock range?
 - Maybe the limits of the VCO adjustment (if this is small).
 - Otherwise, the limits of the phase detector output
 - multiplied by the gain of the filter, k_a
 - multiplied by the frequency sensitivity of the VCO, k_f .




Capture Range

- We define the capture range of the PLL as:
 - The range of input frequencies at which loop can acquire a lock.
 - e.g. if the signal has just been switched on...
- Cannot exceed lock range – usually less
- Depends on bandwidth of loop filter
 - when not locked, phase detector output is at difference frequency
 - must be within bandwidth of loop filter in order to affect VCO frequency
 - with no input, or input far from VCO, VCO runs at centre frequency, f_0




Frequency Synthesis

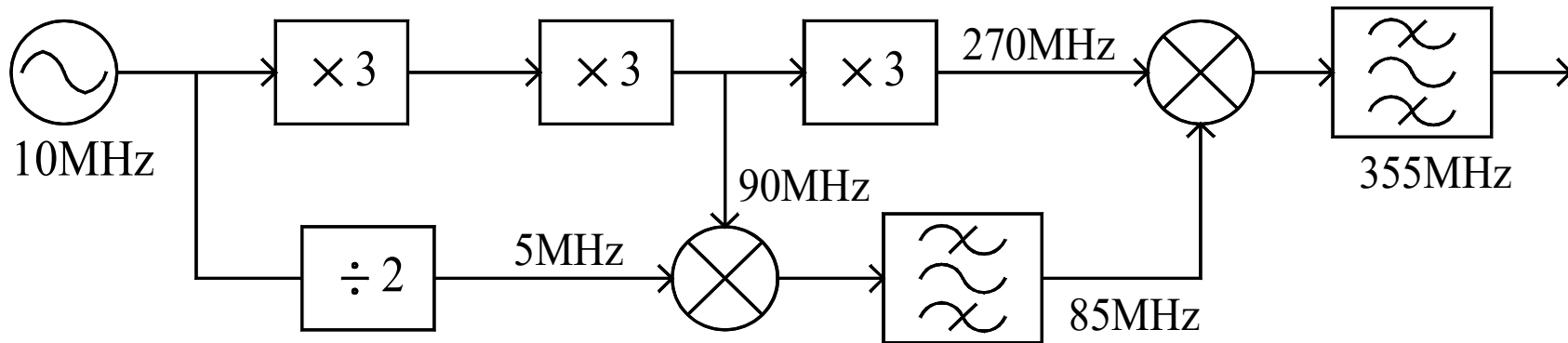

- Generate any one of a discrete set of freq.
 - stability of crystal oscillator
 - agility of VCO
 - usually computer controlled
- Example is original Direct Freq. Synthesis
 - stable crystal oscillator provides input
 - multiply, divide, mix to get desired output
 - switch hardware for adjustable output



Indirect Frequency Synthesis

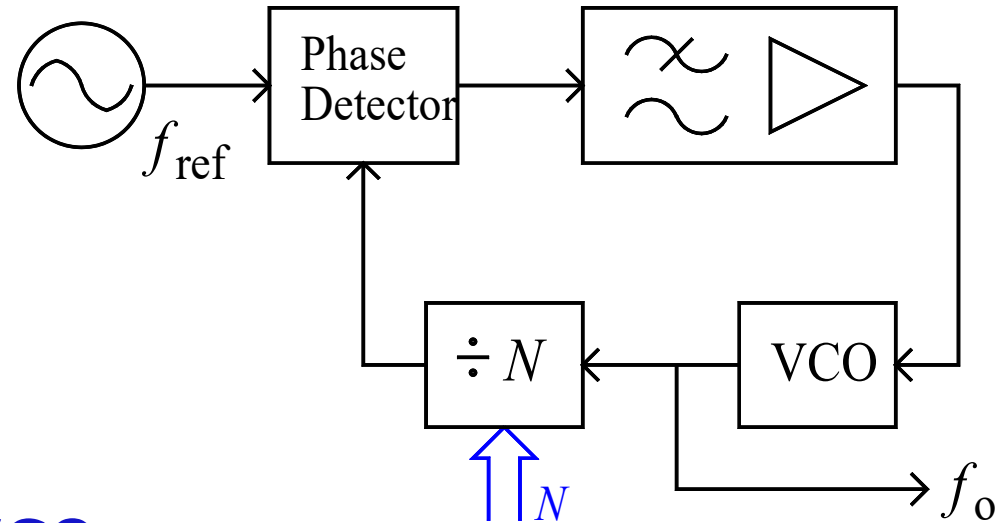

- Output is from VCO

- use PLL to lock frequency to stable reference
- if loop locked, inputs to phase detector must be at same frequency, so

$$f_o = N f_{\text{ref}}$$


- reference frequency derived from crystal osc.
- divider is digital counter, adjustable N
- number-controlled oscillator, step size = f_{ref}
- small step size at high frequency \Rightarrow large N



Problems

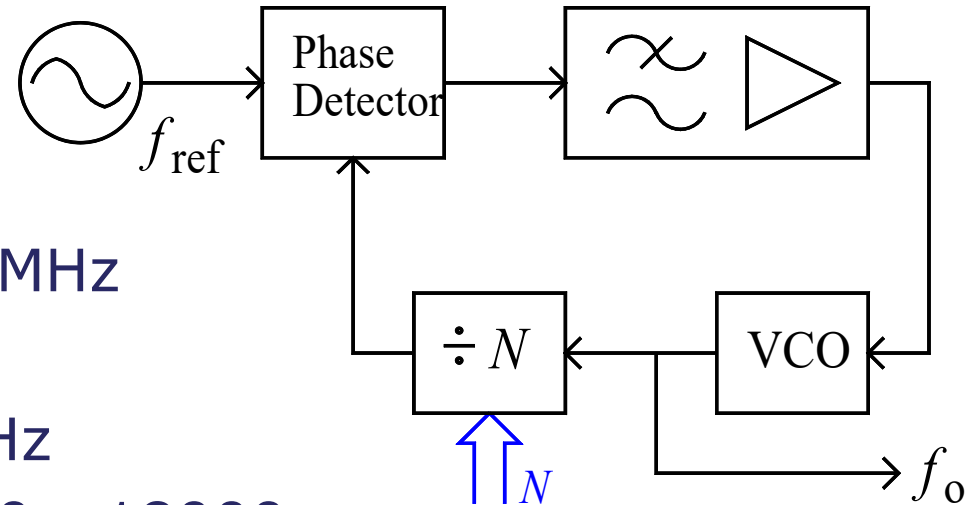- Example:

- want 440 - 450 MHz
- steps of 25 kHz
- need $f_{ref} = 25$ kHz
- N in range 17600 - 18000



- Slow response - long settling time



- phase detector at 25 kHz, narrow loop filter BW
- VCO control voltage cannot change rapidly

- Phase noise poor

- close to f_o , get phase noise of reference $\times N$
- farther out, get phase noise of VCO
 - PLL has no control above loop filter BW



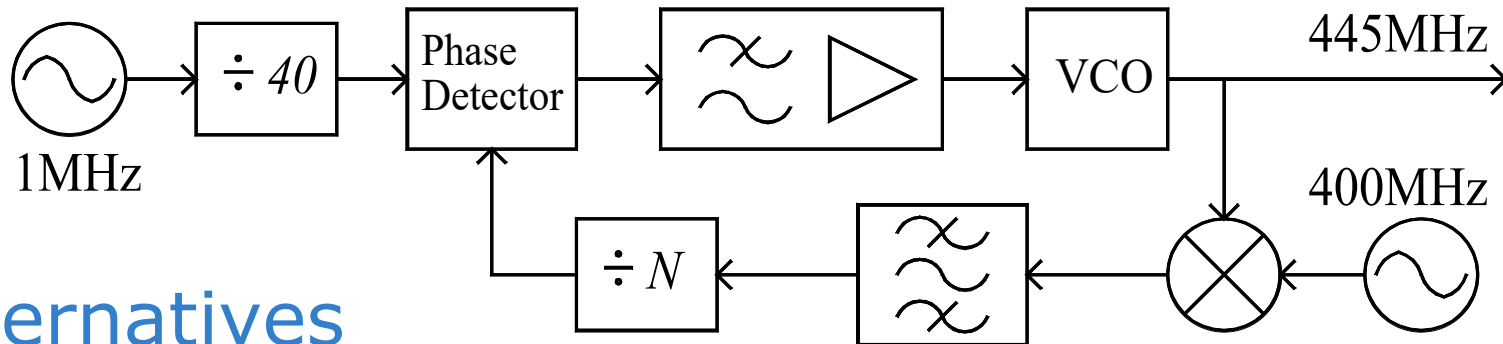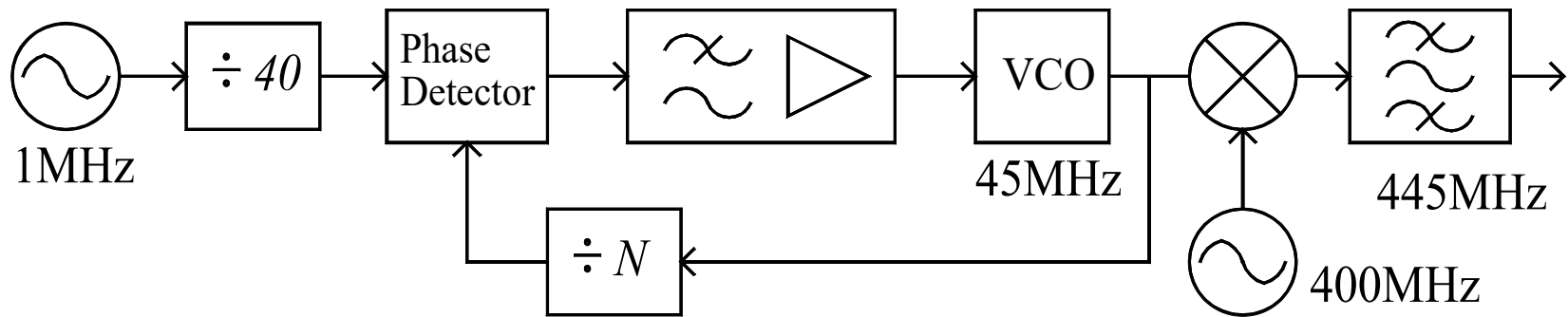
- Hard to build adjustable high-speed divider



Alternatives

- Combine indirect and direct synthesis
 - PLL used to get range and step size, at low freq.
 - add fixed frequency to get required output
 - or run VCO at output frequency,
 - subtract fixed freq. before input to divider

Fractional- N Divider

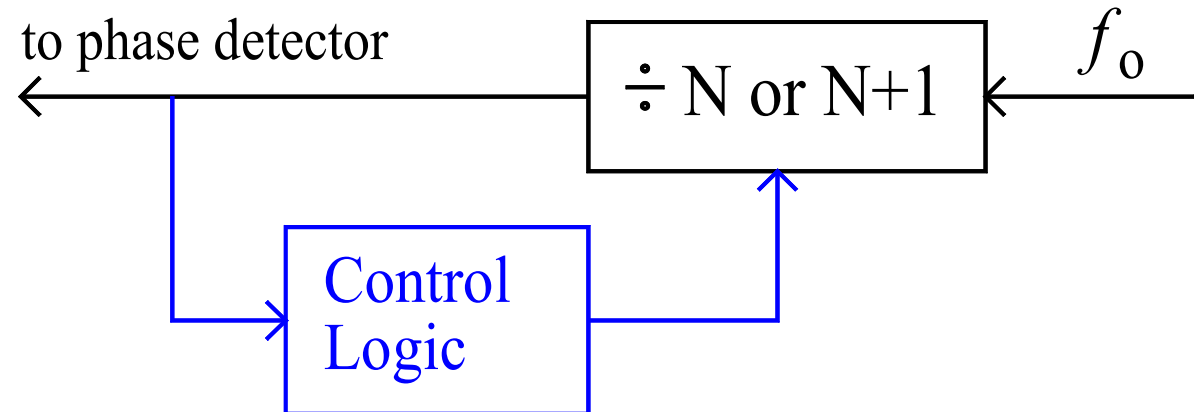


- Modified divider allows non-integer division
 - allows small step size with higher f_{ref}
- High-speed divider, with 2 division ratios
 - *dual-modulus* divider
 - control logic counts output cycles:
 $\div(N+1)$ for k cycles of each R , then
 $\div N$ for $R-k$ cycles of each R

average division ratio =
$$\frac{(N+1)k + N(R-k)}{R} = N + \frac{k}{R}$$



Fractional- N Synthesis

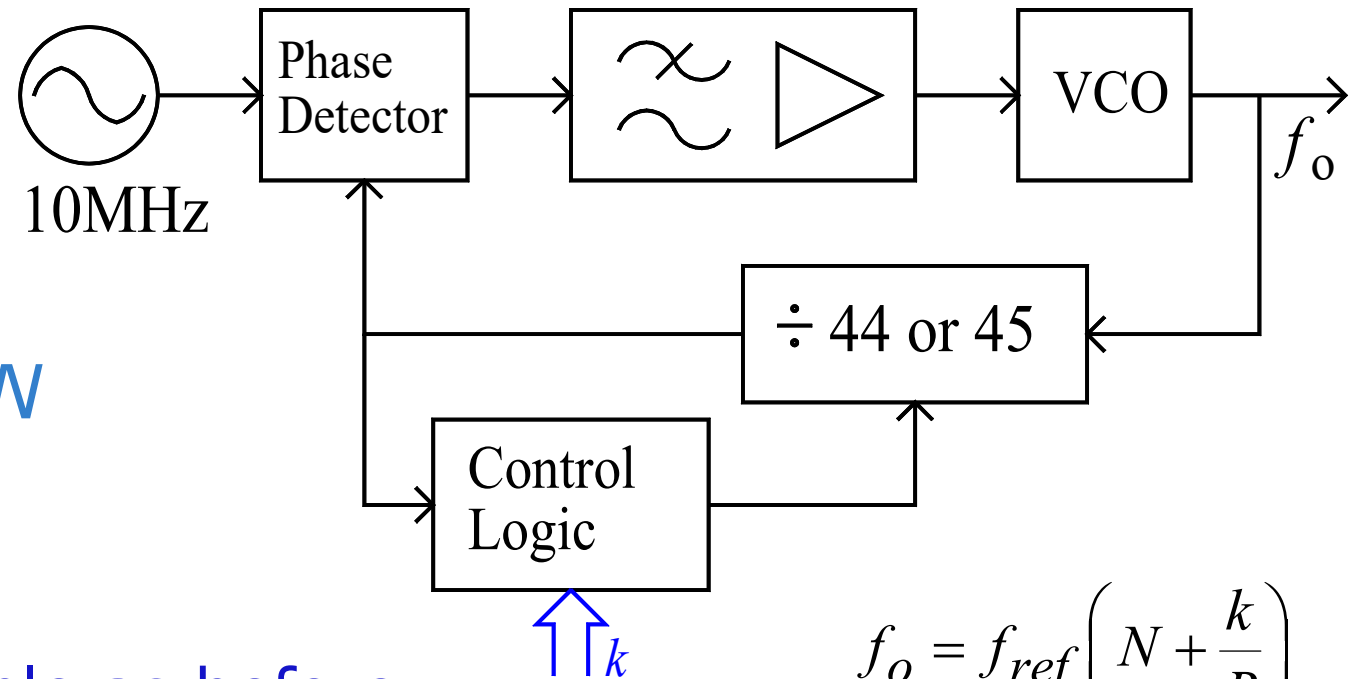

$$f_o = f_{ref} \left(N + \frac{k}{R} \right)$$

- Example as before

- want 440 to 450 MHz, 25 kHz steps
- now use $f_{ref} = 10$ MHz (for example)
 - allows much larger loop filter BW
- Choose N to get frequency in required range
 - here $N = 44$, so minimum output freq. 44 times f_{ref}
- choose R to get required step size ...
- adjust k to get specific frequency

$$f_o = 440 \text{ MHz} + k \times 25 \text{ kHz}$$




Problems


- Spurious components in output
 - note periodic change in division ratio at $\frac{f_{ref}}{R}$
 - \Rightarrow periodic component in VCO control voltage
 - \Rightarrow periodic frequency modulation of VCO
 - \Rightarrow spurious components in output spectrum, at multiples of f_{ref}/R on both sides of f_o .
- Solutions:
 - randomise division adjustment
 - much more complex hardware...
 - add compensating signal to control voltage
 - since error is periodic and predictable...




Double frequency with a d-type flip-flop

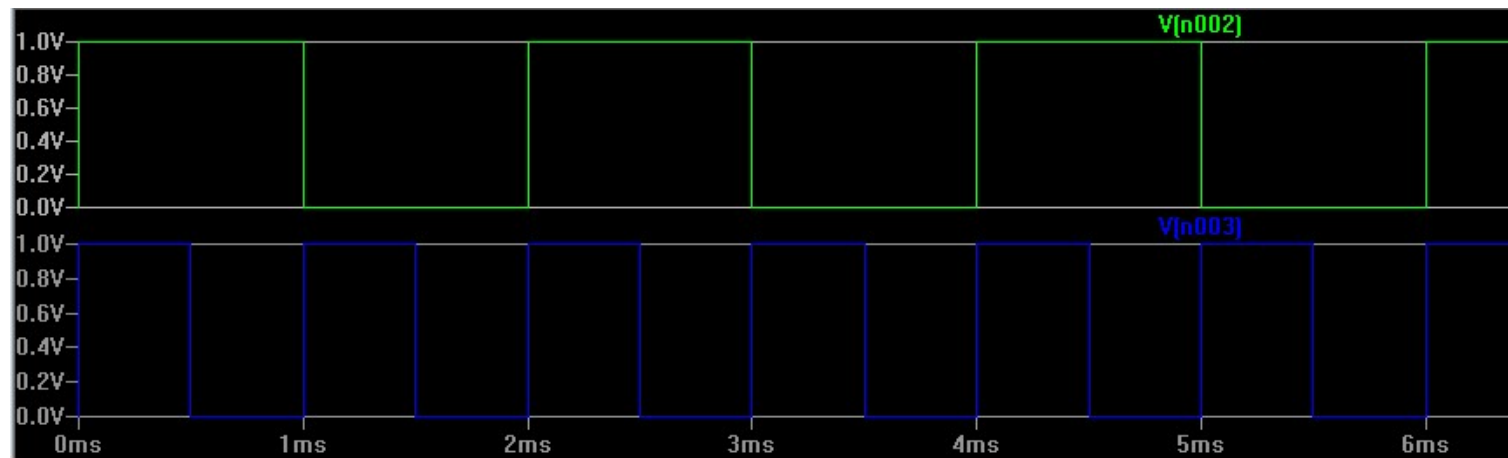

Draft1.asc

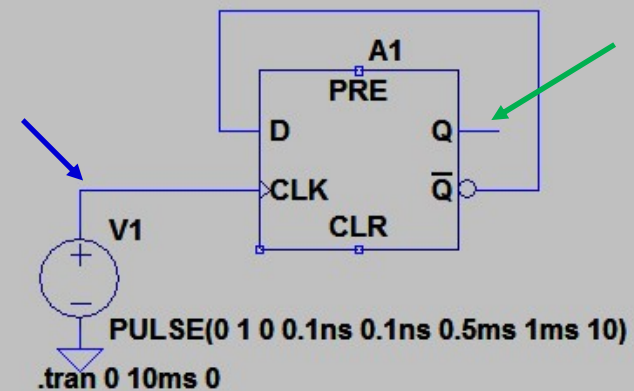

Direct Digital Synthesis

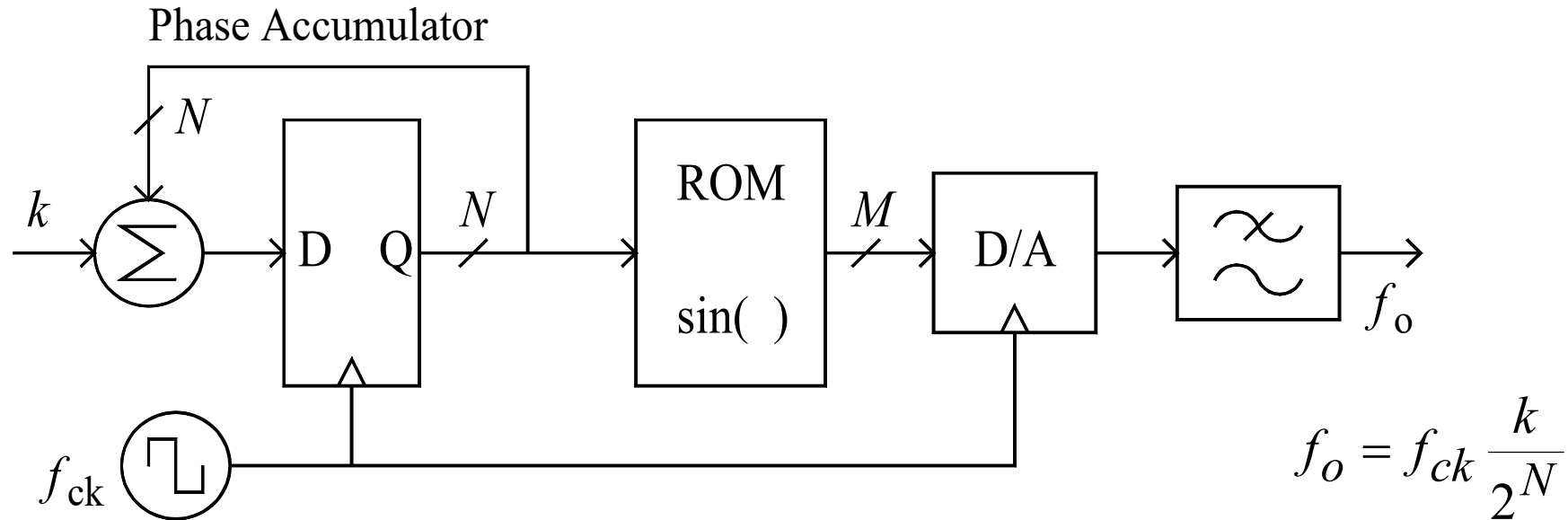


- Generate samples of signal digitally
 - add k to phase accumulator on each clock
 - so phase value advances at adjustable rate
 - overflows regularly - view as angle, 0 to 2π
 - ROM gives $\sin()$ of this phase angle
 - apply samples to D/A converter, reconstruct



DDS


$$f_o = f_{ck} \frac{k}{2^N}$$

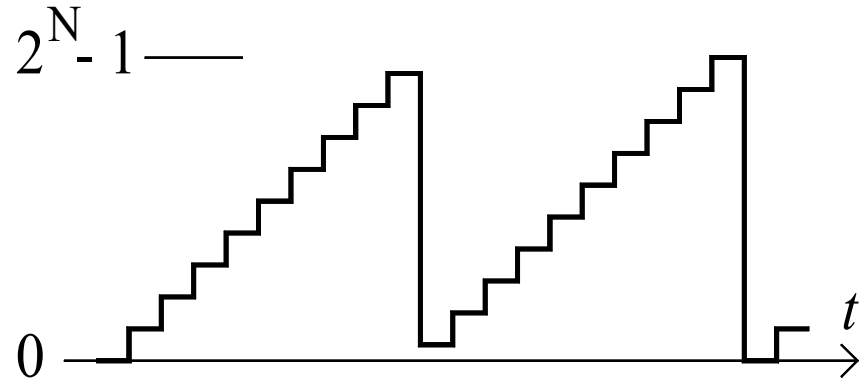

- For large N , extremely small frequency steps
 - low phase noise - due to clock jitter
- Many spurious outputs
 - phase has other periodic components
 - in example above, at half output frequency
 - quantisation errors - also periodic
- Output frequency
 - must be much less than clock frequency
 - also limited by speed of D/A converter
- Modulation possible - phase, frequency



Example: AD9830

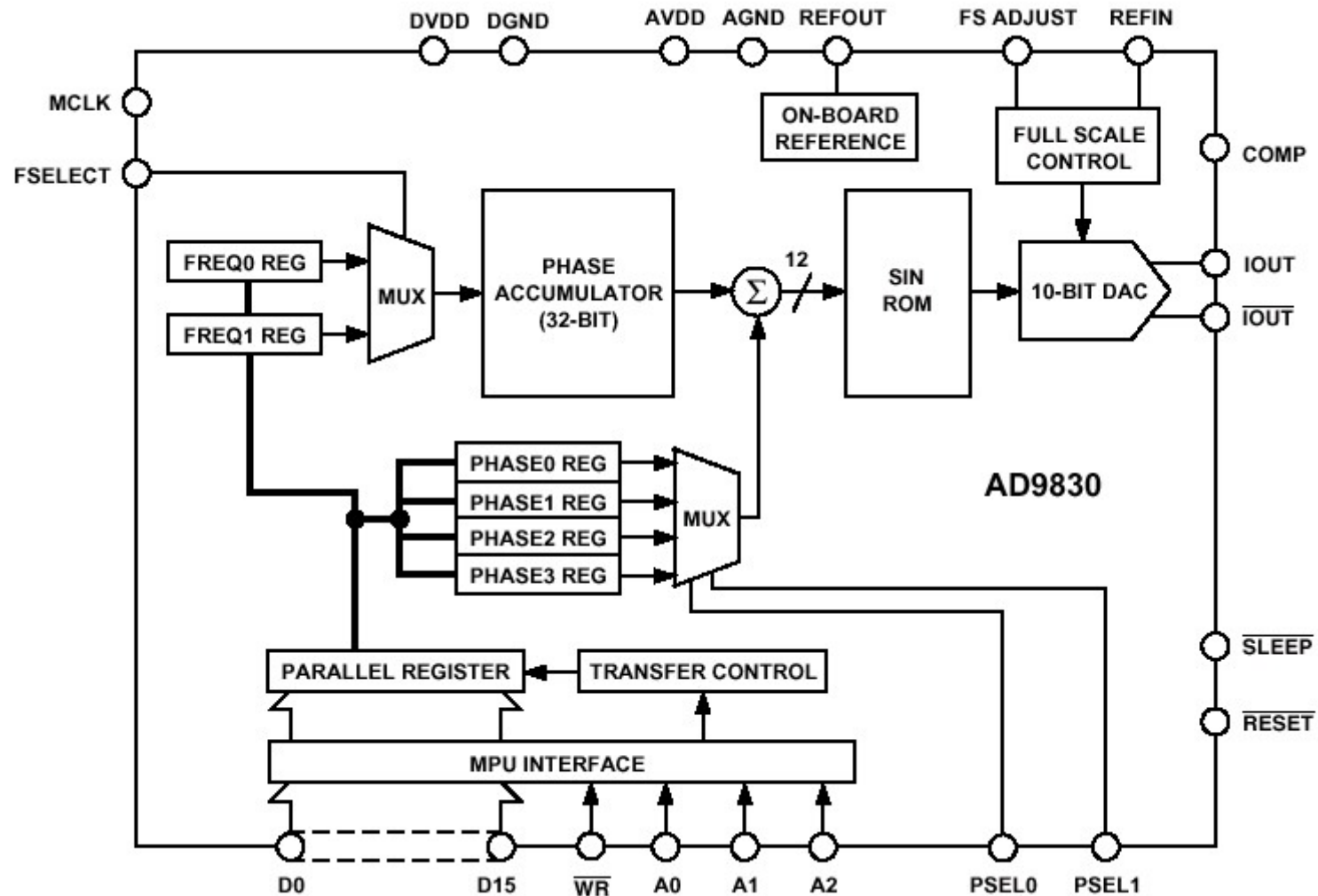

- 50 MHz max clock, 32-bit phase, 10-bit DAC
- 2 frequencies, 4 phase offsets stored

Example: AD9910



- 1 GHz max clock
 - output up to 400 MHz (with good filter)
- 32-bit phase accumulator, 14-bit DAC
 - freq. resolution ~ 0.23 Hz at 1 GHz clock.

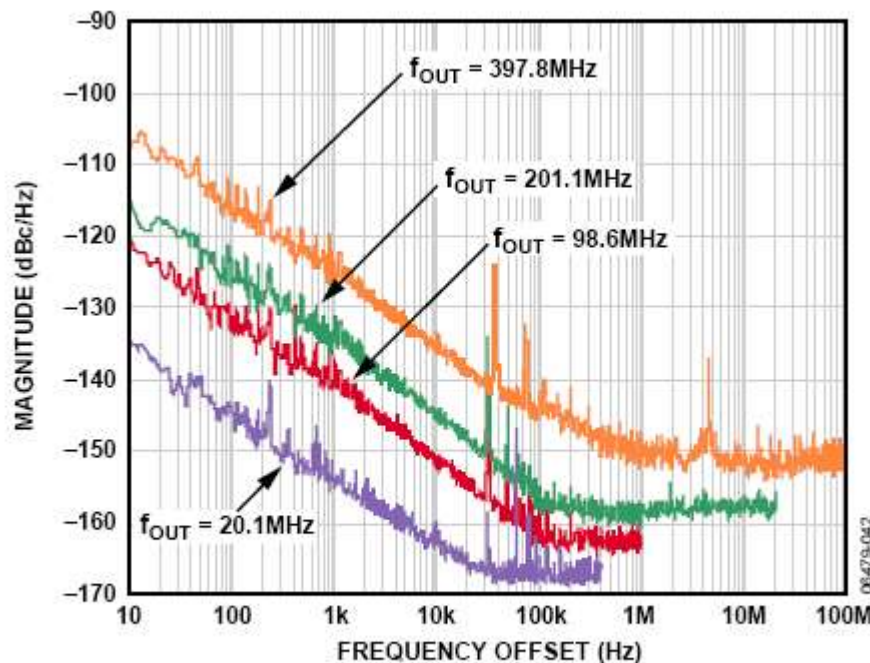


Figure 15. Residual Phase Noise Plot, 1 GHz Operation with PLL Disabled

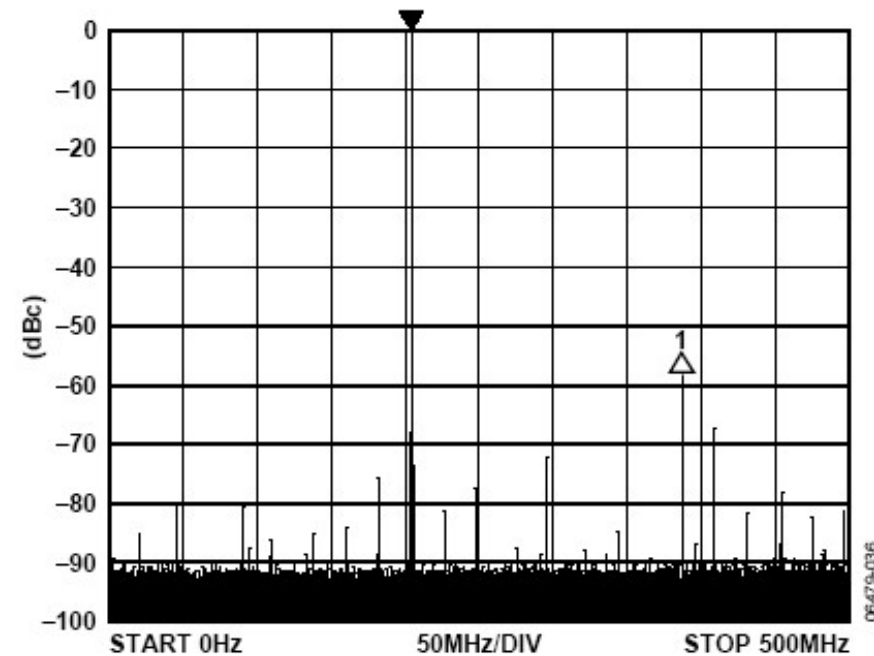


Figure 10. Wideband SFDR at 204 MHz, REFCLK = 1 GHz