

EEEN3006J

# Wireless Systems

*Dr. Declan Delaney*

*(declan.delaney@ucd.ie)*



**Beijing Dublin International College**


# Purpose of the lecture

- In this lecture, we will discuss how to make local oscillators of certain frequency.
- Oscillators are non-linear circuits that take in DC power and output a particular frequency.
- Used in transmitters as:
  - carrier signal into modulator
  - oscillator to drive mixer for up-conversion
- Used in receivers as:
  - local oscillator for mixer for down-conversion
  - local oscillator for demodulation


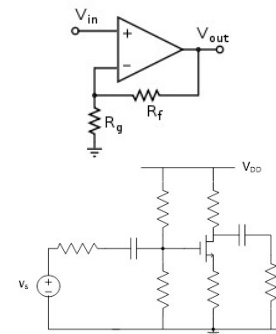
# Purpose of this lecture


- We usually make them using an amplifier with feedback.
  - The amplifier can be made using
    - Op-amps (Only at lower frequencies), or
    - Transistors
- We usually make them using feedback made up of passive RC or LC circuits.
- Later in the lecture, we will see how to take a very stable low-frequency oscillator and make a tuneable high-frequency oscillator from it.


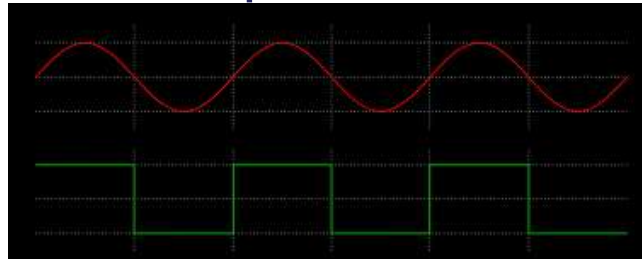
# What makes a good oscillator?




- A periodic signal
  - often sinusoidal signal
  - sometimes a square-wave.



- Frequency may be
  - Fixed value, or
  - controlled by voltage or temperature.
    - VCO = voltage controlled oscillator.

# Need: Frequency Stability

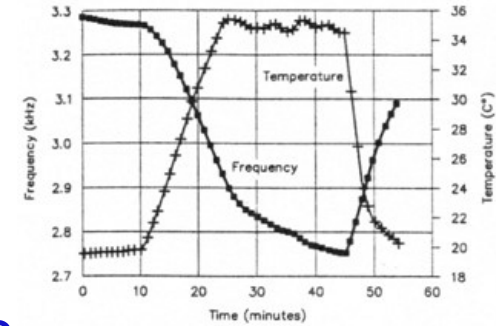


*Temperature drift in a 7-MHz variable-frequency oscillator.  $\sim 10^4$  ppm/°C*

- Average frequency is accurate
  - over time, and
  - over a reasonable temperature range
- The permitted error  $\propto$  signal bandwidth
  - Easy case: baseband signal, large bandwidth.
  - Difficult case: narrow-band, high-frequency.
- We measure:
  - Error, in parts per million (ppm) or parts per billion (ppb).
  - Variation with temperature; ppm/°C or Hz/°C.
  - Ageing; ppm/year.



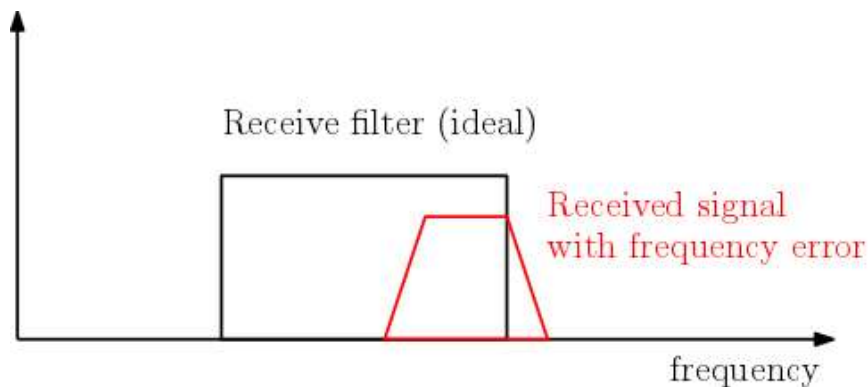- The transmitter needs to transmit at the correct frequency
  - transmit where receiver is expecting signal
  - avoid interference with neighbours
- The receiver needs to shift the frequency of the input signal by the correct amount
  - otherwise wanted signal will not pass through filter.




# Datasheet example
 
## MOFH and MOFZ Series / 14 Pin DIP OCXO



- Oven Controlled Oscillator
- 1.0 MHz to 150.0 MHz Available
- 14-pin DIP Package
- -40°C to 85° Available
- ±50ppb to ±500ppb



### PART NUMBERING GUIDE:

**MOF H 5 S 100 B - Frequency**

**Output Type**  
H = HCMOS  
Z = Sinewave

**Supply Voltage**  
3 = 3.3 Volt  
5 = 5 Volt  
12 = 12 Volt

**Crystal Cut\***  
Blank = AT Cut  
S = SC Cut

**Operating Temperature**  
A = 0°C to 50°C  
B = -10°C to 60°C  
C = -20°C to 70°C  
D = -30°C to 70°C  
E = -30°C to 80°C  
F = -40°C to 85°C  
G = 0°C to 70°C

**Frequency Stability**  
050 = ±50ppb  
100 = ±100ppb  
250 = ±250ppb  
500 = ±500ppb

\*Specific Stabilities/ Temperatures requires an SC Cut Crystal


### ELECTRICAL SPECIFICATIONS:

Frequency Range		1.0 MHz to 150.0MHz		
Frequency Stability		±50ppb to ±500ppb		
Operating Temperature		-40°C to 85°C max*		
* All stabilities not available, please consult MMD for availability.				
Storage Temperature		-40°C to 95°C		
Output	Sinewave	±3 dBm		50Ω
	HCMOS	10% Vdd max 90% Vdd min		30pF
Supply Voltage (Vdd)		3.3V	5V	12V
Supply Current	typ	220mA	200mA	80mA
	max	550mA	400mA	150mA
Warm-up Time		3min. @ 25°C		
Input Impedance		100K Ohms typical		
Crystal		AT or SC Cut options		
Phase Noise @ 10MHZ		SC		AT
10 Hz Offset		-100dBc		-92dBc
100 Hz Offset		-127dBc		-118dBc
1000 Hz Offset		-140dBc		-135dBc
Voltage Control 0 to VCC		±3ppm typ		±10ppm typ
Aging (after 30 days)		±0.5ppm/yr.		±1.5ppm/yr.

### MECHANICAL DETAILS:



## Need: Spectral Purity

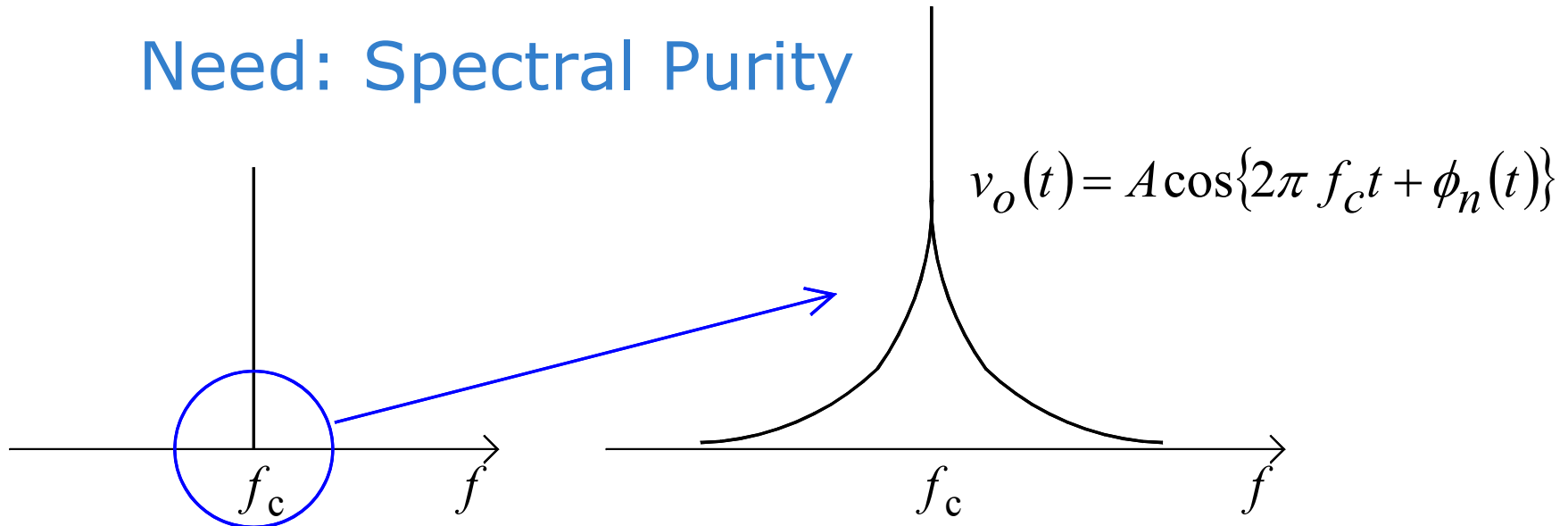

- One line in frequency spectrum
  - no harmonics, no other spurious outputs
- Phase noise = random phase modulation
  - due to random noise in circuit (flicker noise)
  - affects amplitude and phase, but oscillator amplitude control reduces amplitude changes
  - specify power spectral density at some offset
    - e.g. -95 dBc/Hz at 100 kHz
    - dBc = dB relative to carrier (wanted output)



# Often Want Frequency Agility


- Frequency adjustable
  - transmitter works over some range of freq.
  - receiver must receive over some range of freq.
- Specify frequency range, step size
  - step size corresponds to channel spacing
- Speed of adjustment
  - frequency-hopping systems - rapid changes
  - generator settles on new frequency quickly
- Conflict with frequency stability
  - oscillator designed for stability usually not adjustable, certainly not quickly


 
# We make oscillators using feedback

- Oscillators: nonlinear circuits convert DC power to AC.

- Ideally a sinusoid (simpler to design around.)



- Basic idea: amplifier with positive feedback
  - Barkhausen criterion:  $A(j\omega) \cdot \beta(j\omega) = 1 + j0$  at some frequency  $\omega$ .

$$x_o = A x_i + A \beta x_o$$


$$x_o = \frac{A}{1 - A \beta} x_i$$



Barkhausen criterion  
makes the  
denominator zero.


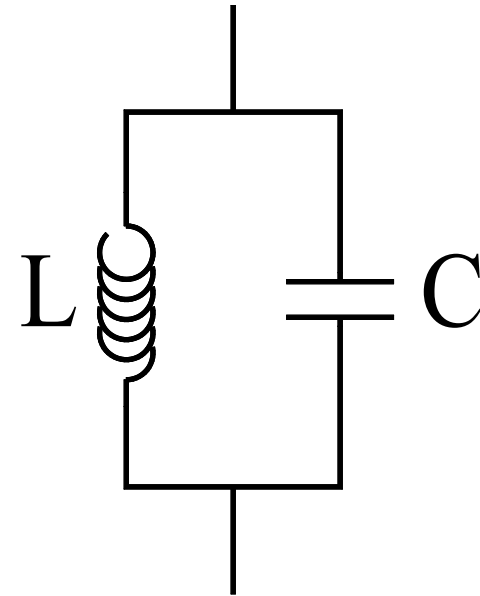
# Basic sinusoidal oscillator

- need narrow bandwidth for spectral purity
  - could use L-C resonant circuit (high Q factor)?
  - for narrower bandwidth, use mechanical resonator
- some non-linearity controls amplitude
  - usually in amplifier






# Quartz Crystal Resonator

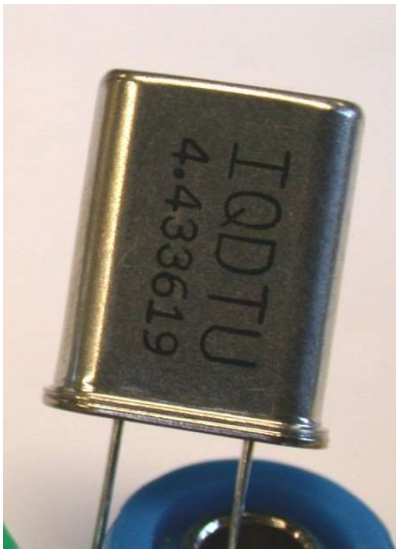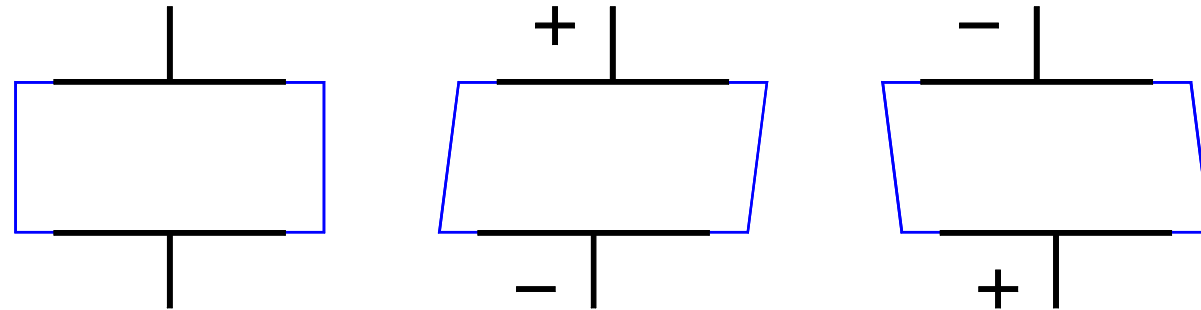

- Quartz exhibits piezo-electric effect
  - applied voltage causes shape change
  - shape change generates voltage
- Crystal acts as mechanical resonator
  - 2 electrodes, piezo-electric conversions
  - effect is electrical resonator
  - high Q-factor:  $10^4$  up to  $10^6$  possible
- Dimensions control resonant frequency
  - up to 100 MHz commonly available


# Quartz Resonator

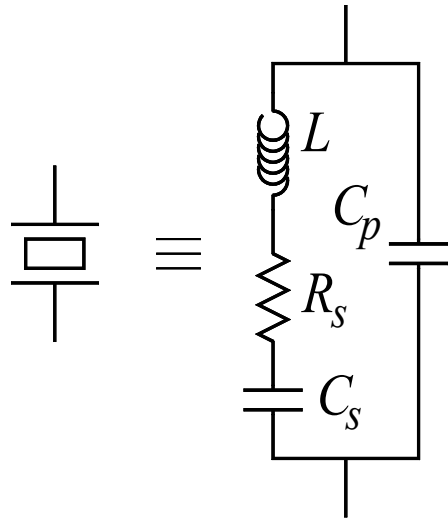

$$\omega_s = \frac{1}{\sqrt{LC_s}}$$

$$\omega_p = \frac{1}{\sqrt{LC'}}$$


$$C' = \frac{C_p C_s}{C_p + C_s}$$

 

- Mechanical resonator, so model:
  - momentum as large inductance ( $L$ , H)
  - elasticity as series capacitance ( $C_s$ , fF)
  - Damping and loss as small series resistance  $R_s$
  - also real capacitance between electrodes (pF)
- series and parallel resonances, very close



# Precision Oscillator

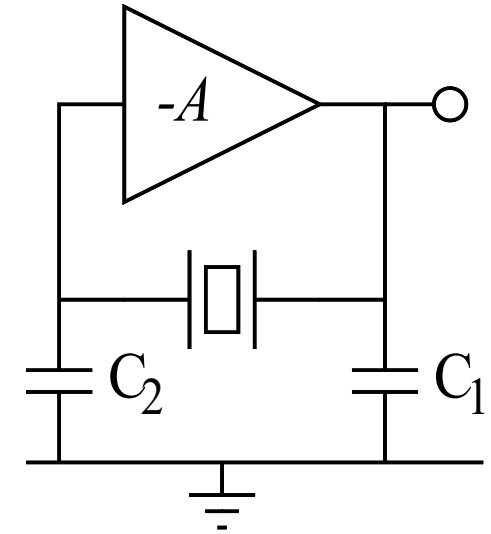


- Want precise frequency, stability, low phase noise
  - use quartz crystal resonator in feedback
    - external capacitors add to parallel capacitance...
    - allow very limited frequency adjustment - ppm
  - for higher precision, place oscillator in oven
    - temperature controlled chamber – TCXO
- Other mechanical resonators possible
  - ceramic resonators
    - similar to quartz, but not as good
  - surface acoustic wave (SAW) resonators
    - vibrations on surface, not in bulk of material




# Voltage-Controlled Oscillator


$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

 

- At RF, usually LC resonant circuit
  - poor precision - Q-factor  $\sim 10^2$
  - (L could be transmission line stub)
- Need electrical adjustment
  - often use capacitance change in diode
  - reverse-biased by control voltage
  - special diodes are optimised for this
  - non-linear relationship
- Easy, quick to change frequency
  - limited range of adjustment
  - difficult to get precise frequency

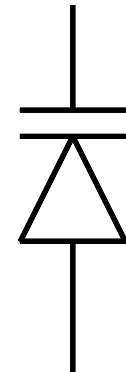

## Example: Hartley Oscillator


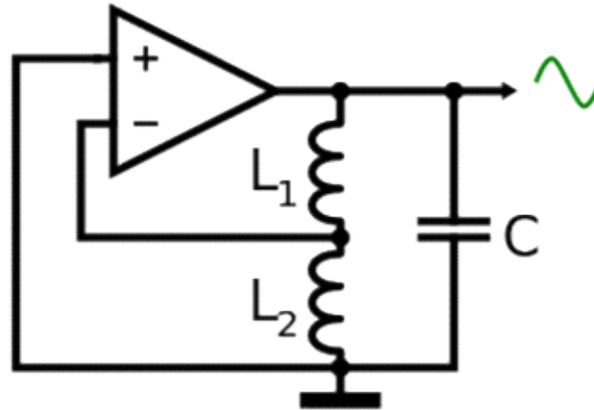


This diagram shows a variant which uses an op—amp, but transistor-based designs are also common.

- Basic oscillator uses 2 inductors & 1 capacitor
  - can also use 1 tapped inductor (mutual  $L$ )
- Modify for Voltage Controlled Oscillator – replace capacitor with varactor
  - extra capacitor (large) to isolate varactor bias
  - large inductance, “RF choke”, to isolate signal




## Example: Multi-vibrator

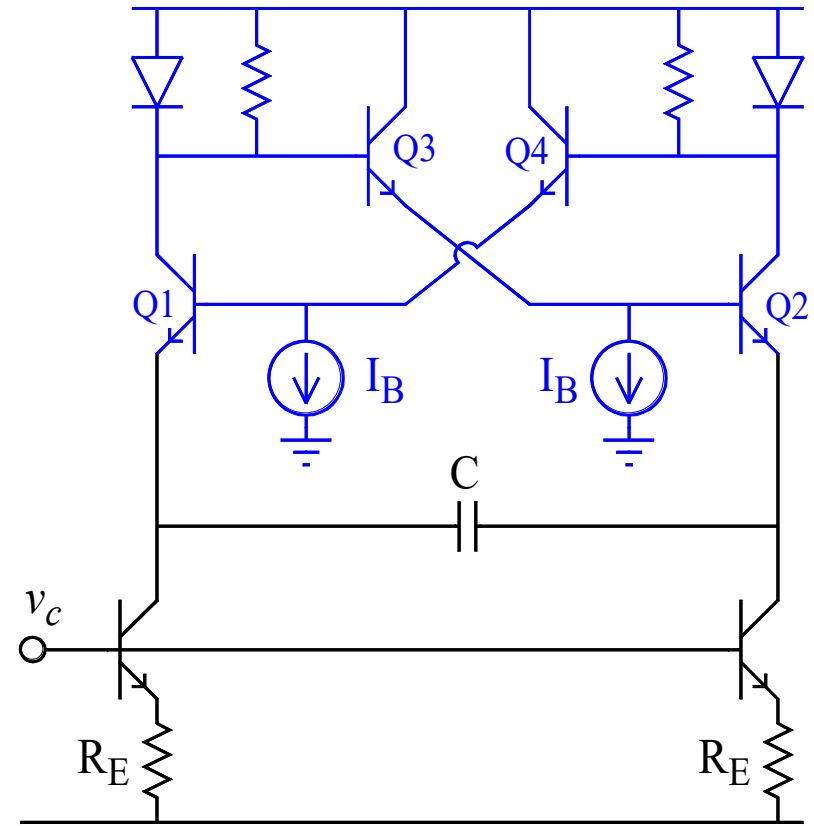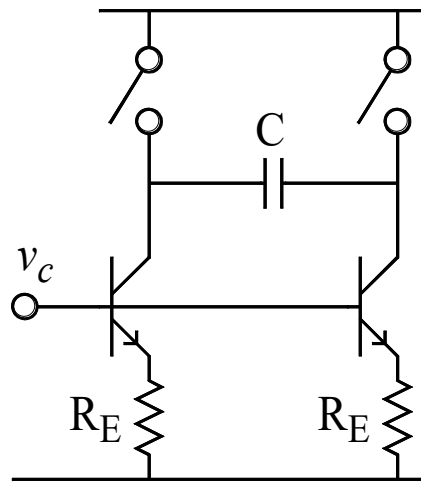

- Capacitor alternately charged & discharged
  - voltage-controlled current sources set freq.
  - switches change charging direction
- More suitable for IC implementation
  - but not at very high frequencies...




# Frequency Scaling

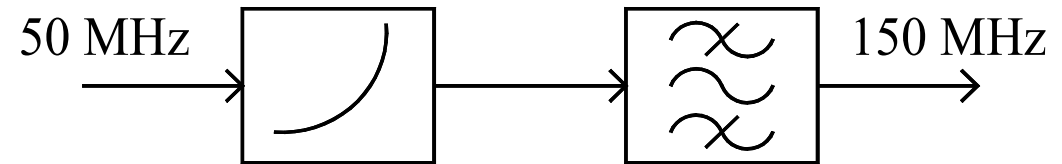

- Multiplication
  - use non-linear device to generate harmonics
  - band-pass filter to select required frequency
  - also multiplies phase noise
- Division
  - use flip-flops, counters, etc. to divide by  $N$
  - square-wave output (could filter for sine)
  - also divides phase noise
- Addition, subtraction
  - use mixer as seen already (frequency shifting)



# Phase-Locked Loop (PLL)

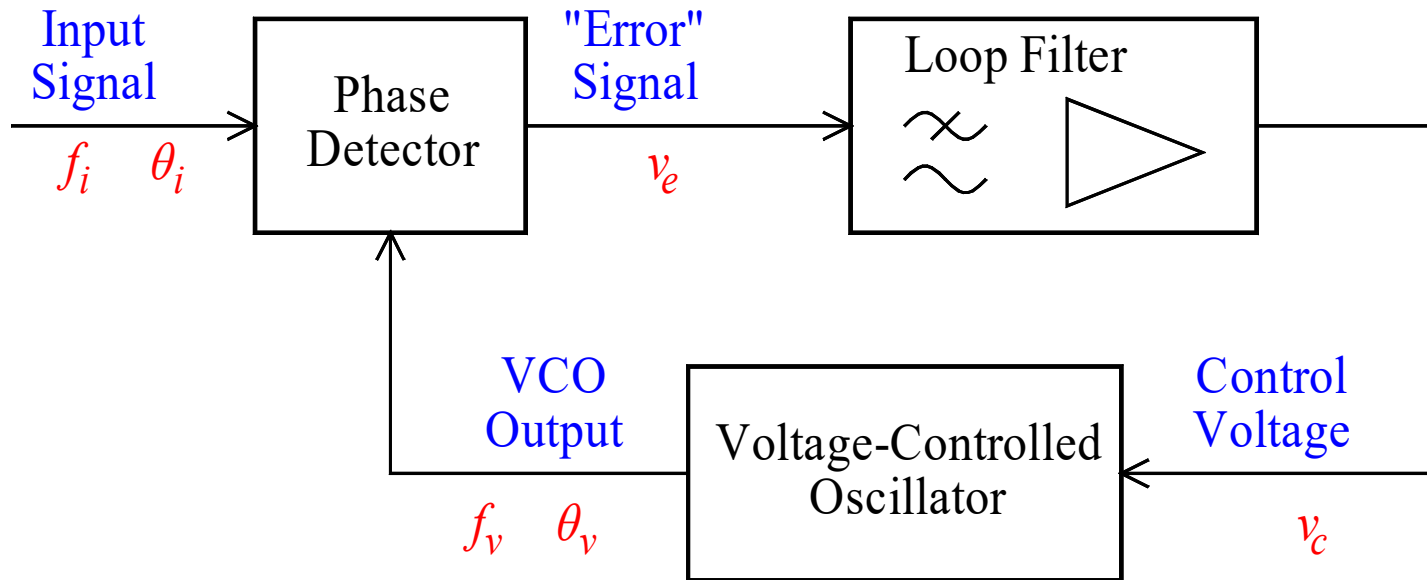

- Feedback control system
  - adjusts frequency of VCO to match input
  - phase detector measures phase difference
  - loop filter provides gain and low-pass filter
    - controls behaviour of the system





# PLL Application Examples

- Noisy or modulated input
  - want VCO to follow average frequency of input
  - use loop filter with narrow bandwidth
  - in communications receiver, extract carrier frequency or clock frequency from signal...
- Frequency Modulation – demodulator
  - get VCO to follow changing input frequency
  - loop filter bandwidth must be wide enough
  - then control voltage  $\propto$  modulation...
- Frequency Synthesis
  - input from stable (e.g. crystal) oscillator
  - synchronise VCO with multiple of input freq.
  - get agility of VCO with stability of crystal...




# Phase Detector Example 1

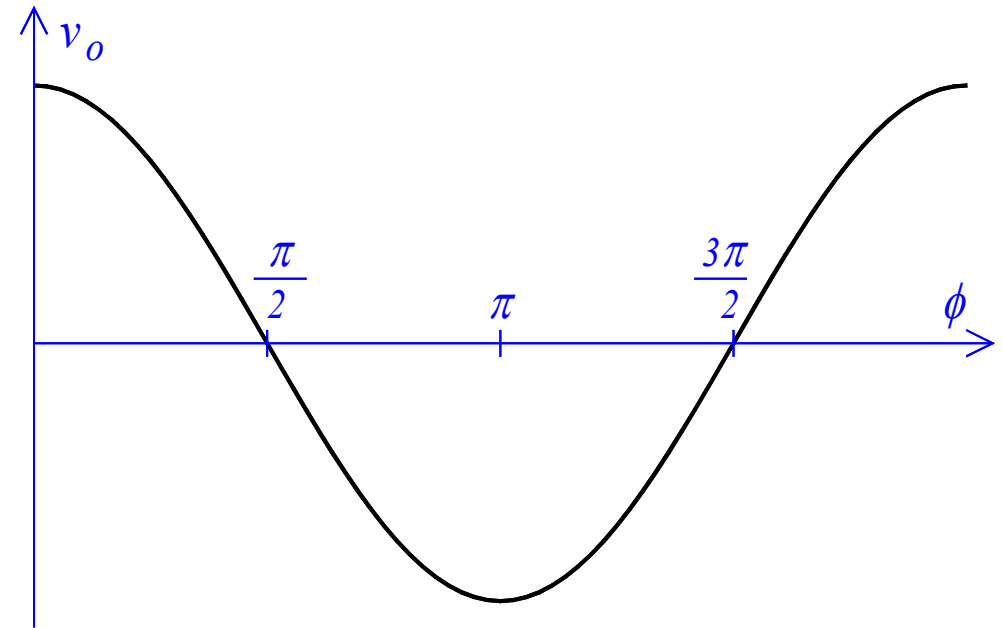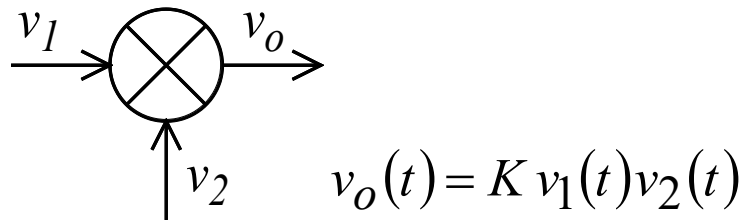

- Ideal Multiplier
  - inputs  $v_1(t) = A_1 \sin(\omega_1 t)$      $v_2(t) = A_2 \sin(\omega_2 t + \phi)$
  - $v_o(t) = K \frac{A_1 A_2}{2} [\cos\{(\omega_2 - \omega_1)t + \phi\} - \cos\{(\omega_2 + \omega_1)t + \phi\}]$
  - high-frequency term removed by loop filter...
- If both frequencies equal (PLL is working properly)
  - effective  $v_o(t) = K \frac{A_1 A_2}{2} [\cos(\phi)]$
- non-linear relationship phase difference  $\leftrightarrow$  output
  - $\sim$  linear around zero output




## Phase Detector Example 2

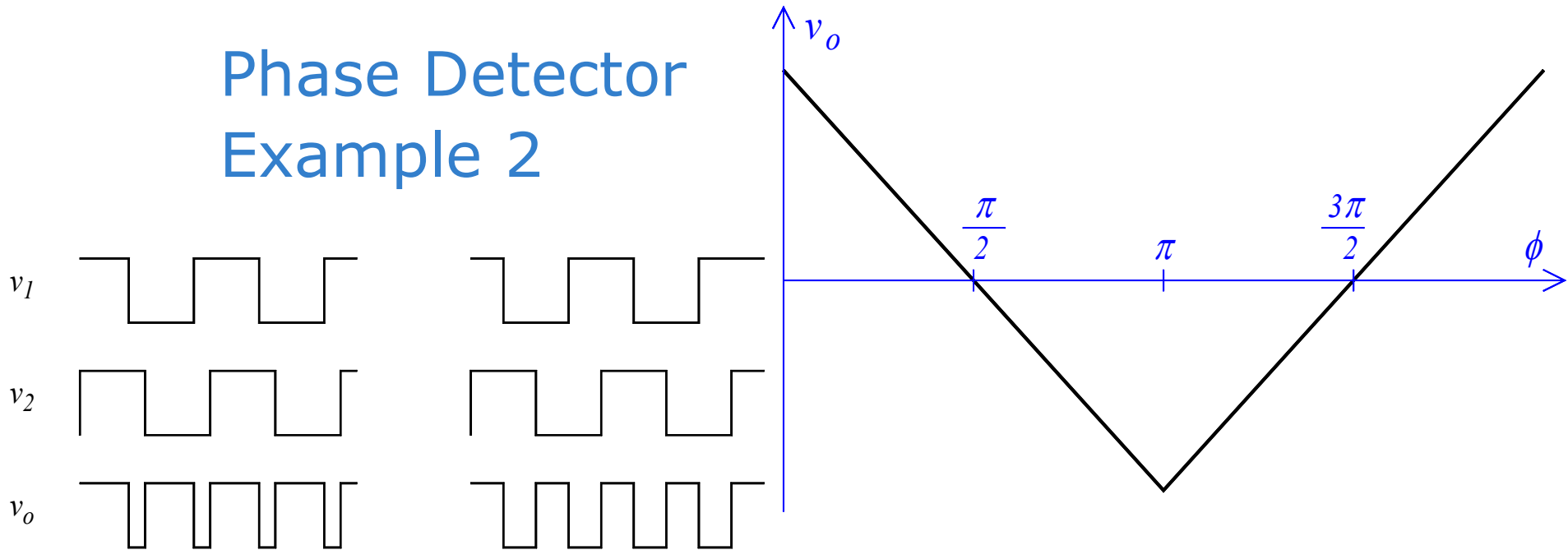

- Multiplier with square-wave signals:  $\pm 1$  V
  - exclusive-NOR gate behaves similarly
- For “phase” difference  $\phi$ , average output
 
$$\overline{v_o} = \frac{K(\pi - |\phi|) - K|\phi|}{\pi} = K \left( 1 - \frac{2|\phi|}{\pi} \right) \text{ assuming same freq.}$$
  - note linear over  $180^\circ$  range
  - periodic in phase difference (as expected)


# PLL Operation

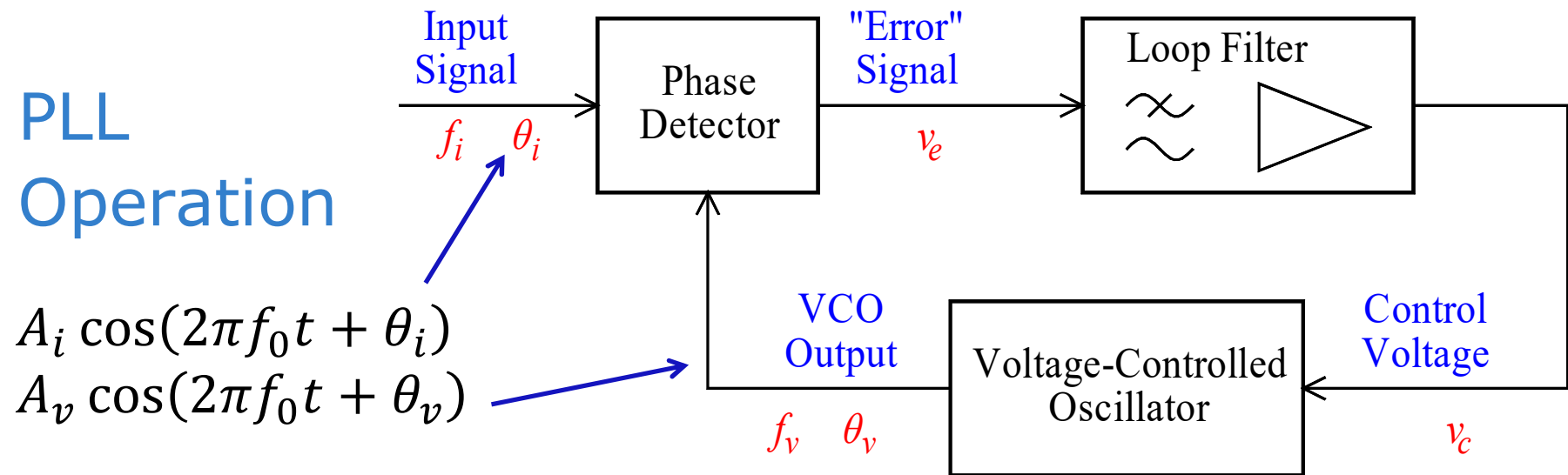

- VCO:  $f_v = f_0 + k_f v_c$      $f_v = f_0 + \frac{1}{2\pi} \frac{d\theta_v}{dt}$ 
  - centre frequency  $f_0$ , change proportional to  $v_c$
  - frequency  $\propto$  rate of change of phase angle
- In normal operation, loop is "locked"
  - $\Rightarrow$  VCO is following frequency of input signal
- If input signal at frequency  $f_0$ 
  - VCO also at  $f_0$ , so  $v_c = 0$ , so  $v_e = 0$
  - so phase difference must be  $\pm \frac{\pi}{2}$




# Stable Operation?

 

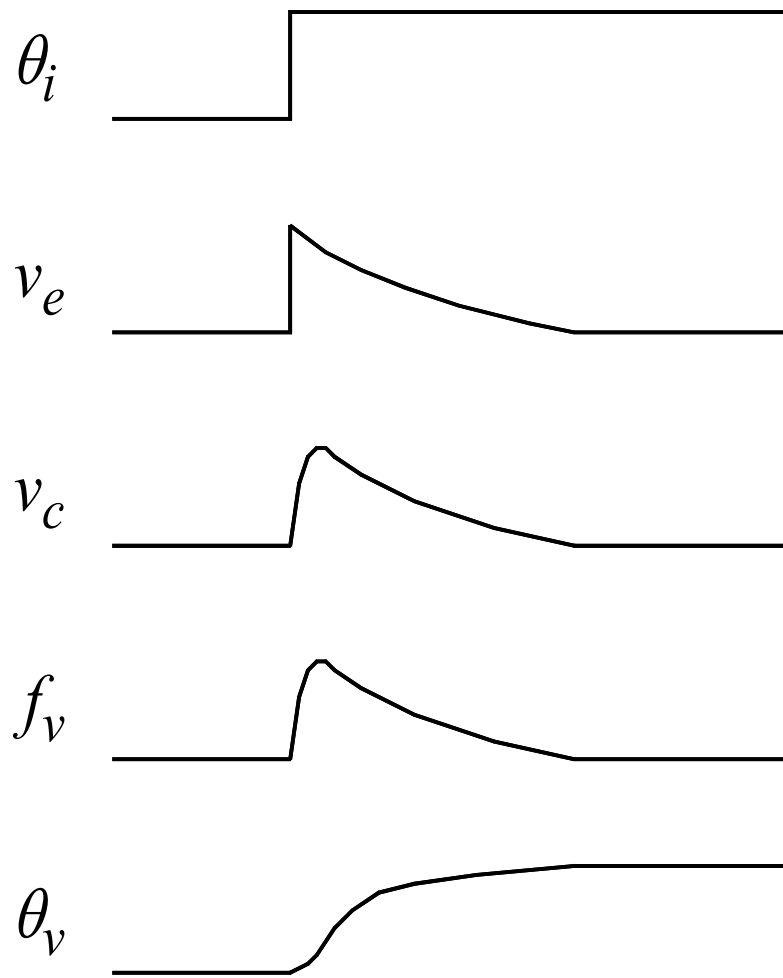- Define phase difference  $\phi = \theta_i - \theta_v$
- Suppose relative phase of input advances
  - $\phi$  becomes larger – moving to right on graph
  - what happens to error voltage?
  - what happens to VCO control voltage?
  - what happens to VCO frequency?
  - what happens to VCO phase?
- Which operating point is stable?








$$\theta_v = \theta_0 + 2\pi \int_0^t f_v dt$$




## Response to Phase Change

- Step change in  $\theta_i$
- $\Rightarrow$  step in  $v_e$
- $\Rightarrow v_c$  starts to rise
  - low-pass loop filter...
- so  $f_v$  follows – VCO
- so phase advances
  - $\Rightarrow$  phase error falls...
- Settles at  $v_c = 0$  again
- transient is example
  - depends on loop & filter parameters

# Phase Change Example

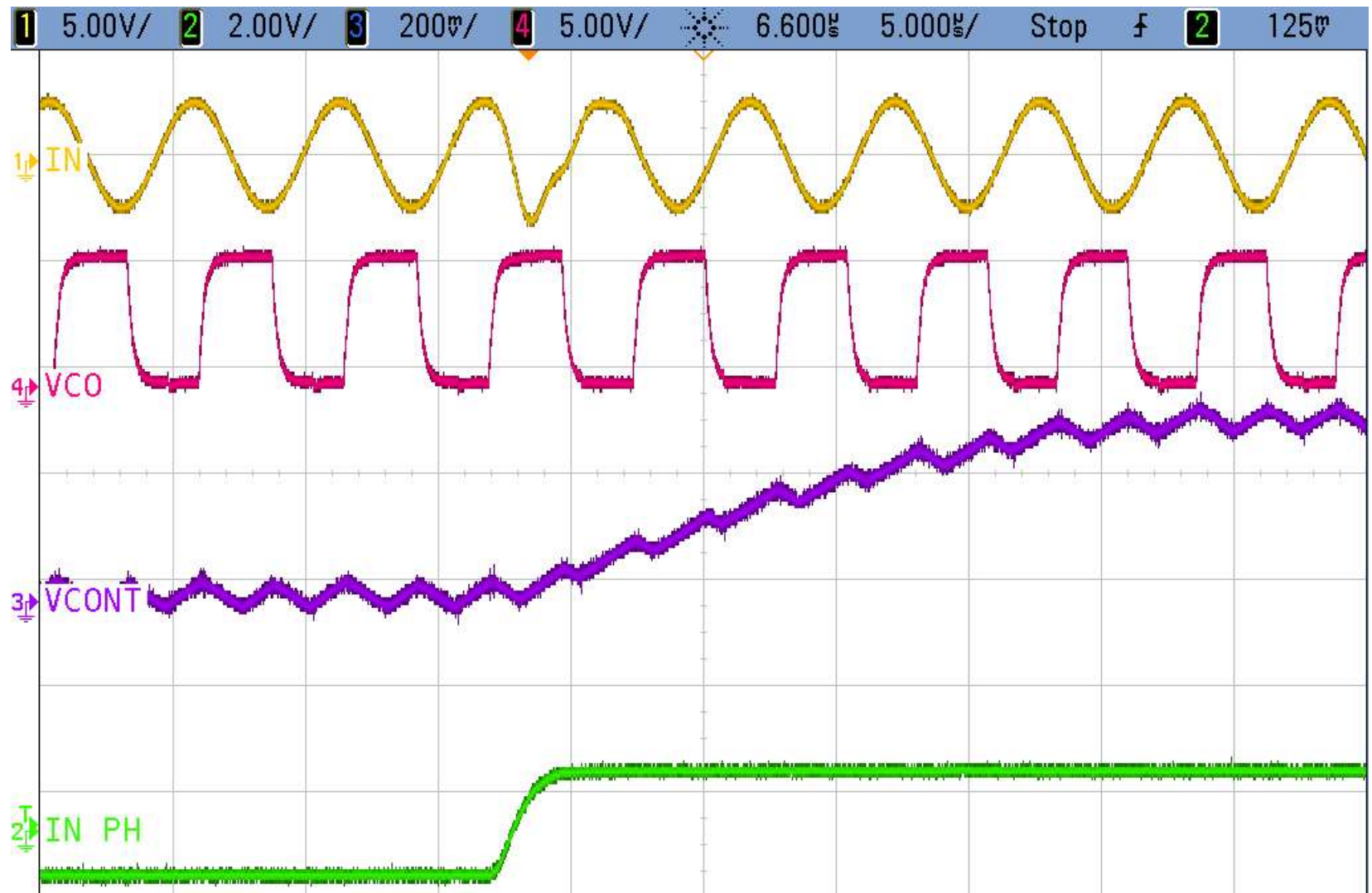


 

## Response to Frequency Change

- Step change in  $f_i \rightarrow f_0 + \Delta f$ 
  - so  $\theta_i$  starts to advance
  - $v_e$  increases
  - $f_v$  follows
  - so  $\theta_v$  advances also
- Settles with  $v_c \neq 0$ 
  - needed to get higher  $f_v$
  - so phase error needed...
- Transient is example

# Frequency Change Example

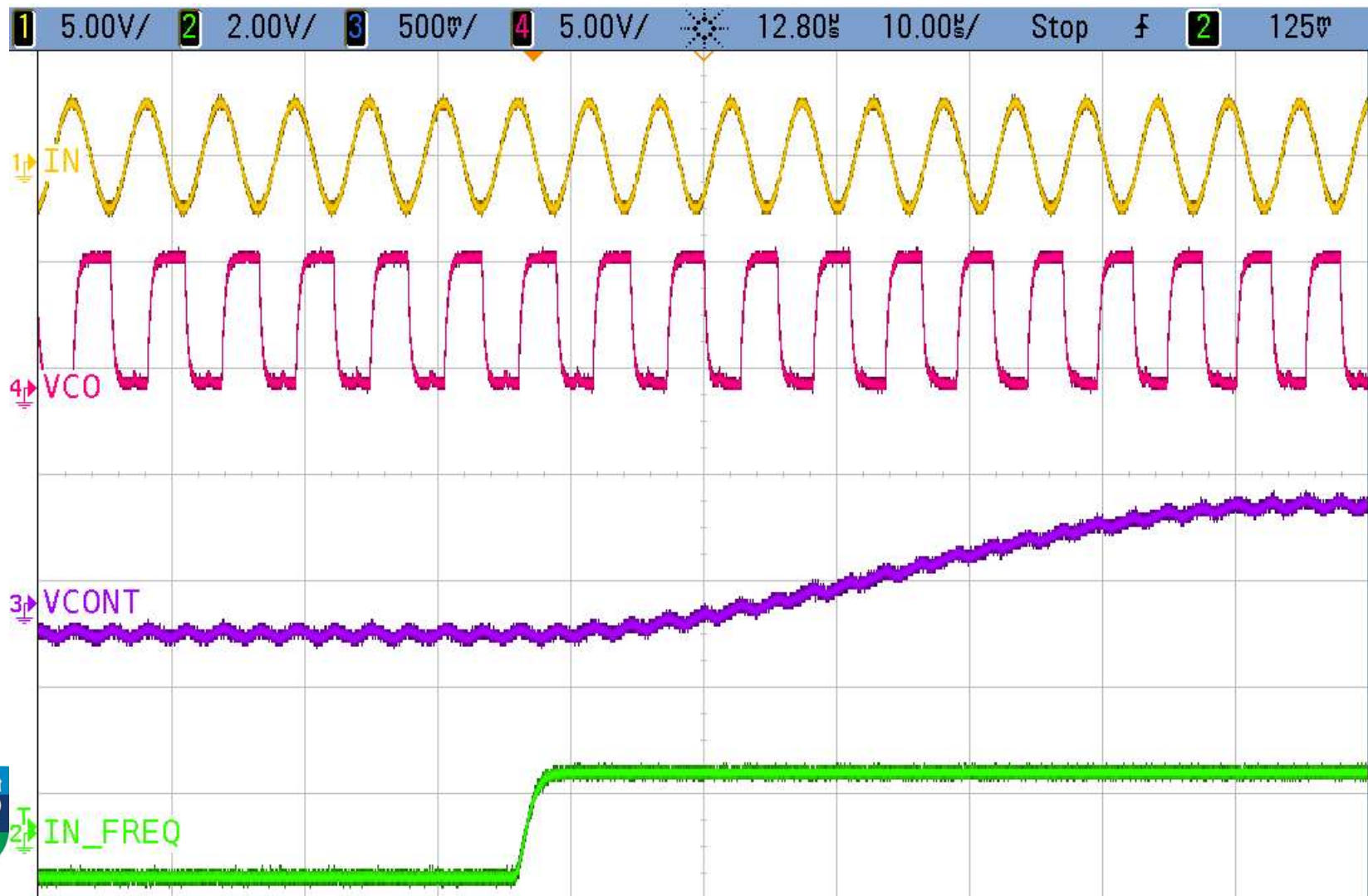

# Lock Range

- We define the lock range of PLL as:
  - range of input frequency over which loop can remain locked.
- What determines the lock range?
  - Maybe the limits of the VCO adjustment (if this is small).
  - Otherwise, the limits of the phase detector output
    - multiplied by the gain of the filter,  $k_a$
    - multiplied by the frequency sensitivity of the VCO,  $k_f$ .




# Capture Range

- We define the capture range of the PLL as:
  - The range of input frequencies at which loop can acquire a lock.
  - e.g. if the signal has just been switched on...
- Cannot exceed lock range – usually less
- Depends on bandwidth of loop filter
  - when not locked, phase detector output is at difference frequency
  - must be within bandwidth of loop filter in order to affect VCO frequency
  - with no input, or input far from VCO, VCO runs at centre frequency,  $f_0$




# Frequency Synthesis

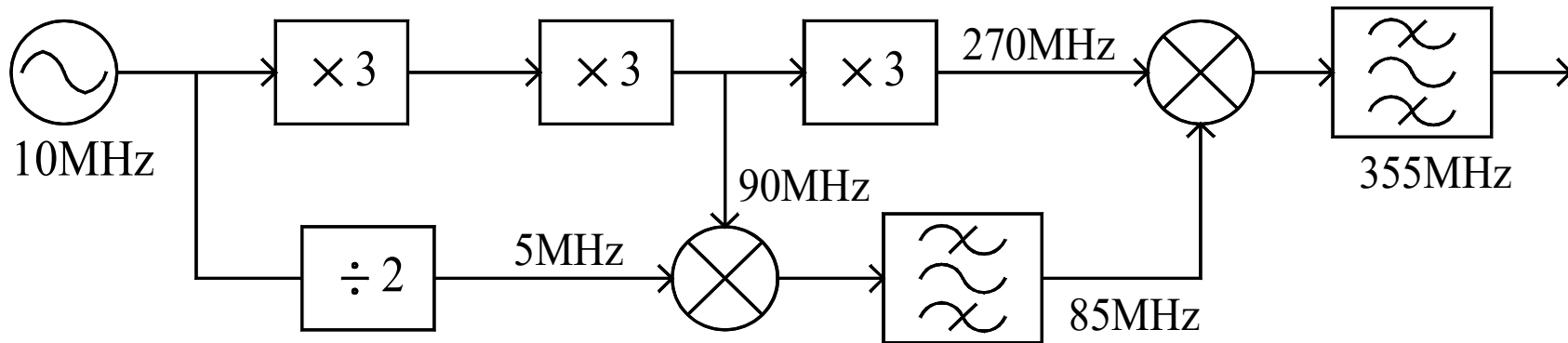

- Generate any one of a discrete set of freq.
  - stability of crystal oscillator
  - agility of VCO
  - usually computer controlled
- Example is original Direct Freq. Synthesis
  - stable crystal oscillator provides input
  - multiply, divide, mix to get desired output
  - switch hardware for adjustable output



# Indirect Frequency Synthesis

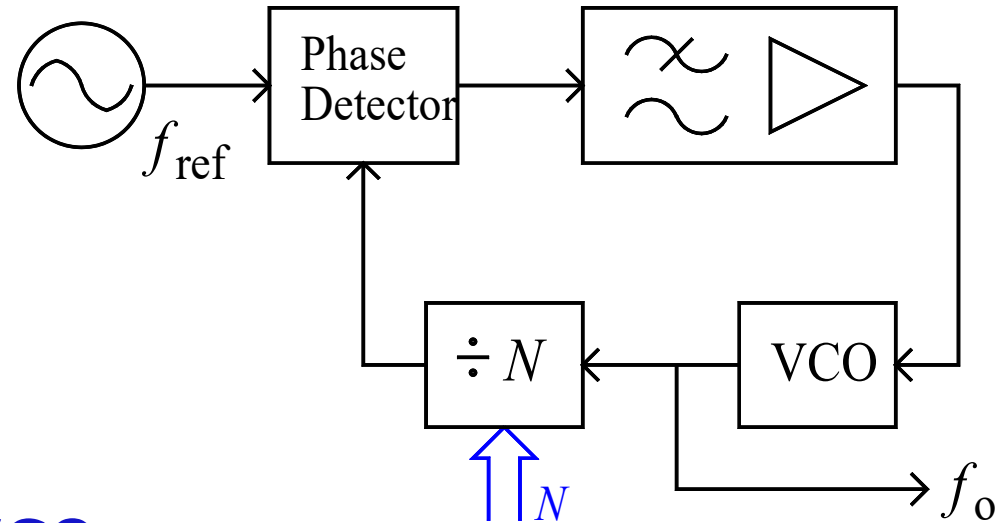

- Output is from VCO

- use PLL to lock frequency to stable reference
- if loop locked, inputs to phase detector must be at same frequency, so

$$f_o = N f_{\text{ref}}$$

- reference frequency derived from crystal osc.
- divider is digital counter, adjustable  $N$
- number-controlled oscillator, step size =  $f_{\text{ref}}$
- small step size at high frequency  $\Rightarrow$  large  $N$






## Problems

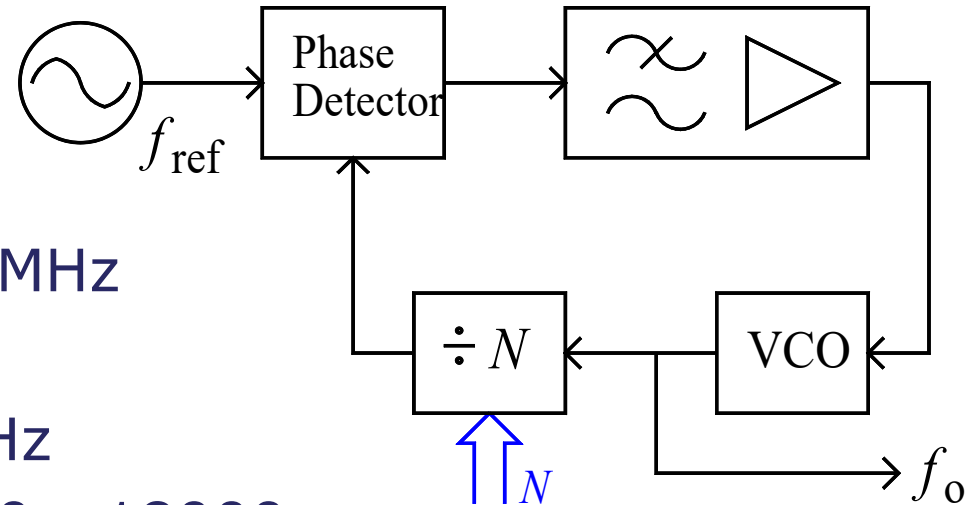- Example:

- want 440 - 450 MHz
- steps of 25 kHz
- need  $f_{ref} = 25$  kHz
- $N$  in range 17600 - 18000



- Slow response - long settling time



- phase detector at 25 kHz, narrow loop filter BW
- VCO control voltage cannot change rapidly

- Phase noise poor

- close to  $f_o$ , get phase noise of reference  $\times N$
- farther out, get phase noise of VCO
  - PLL has no control above loop filter BW



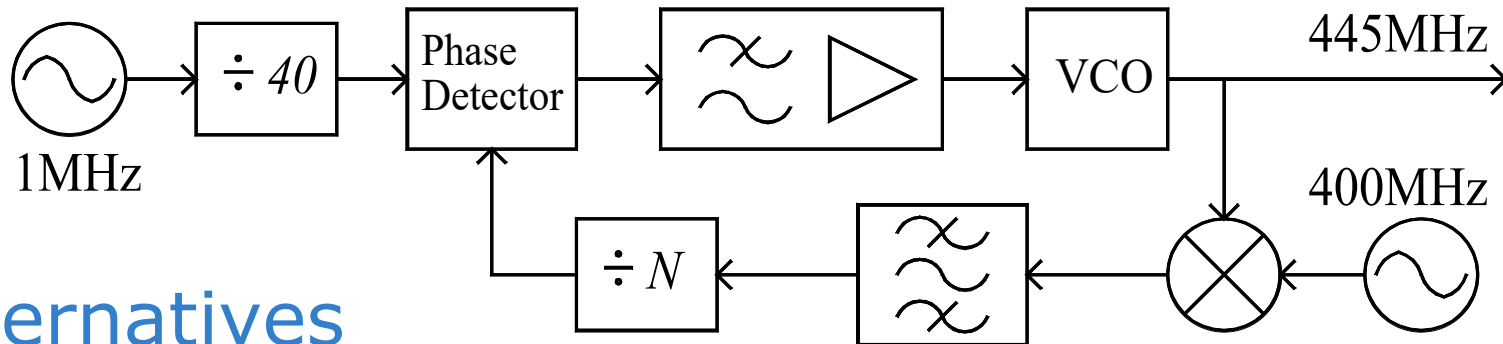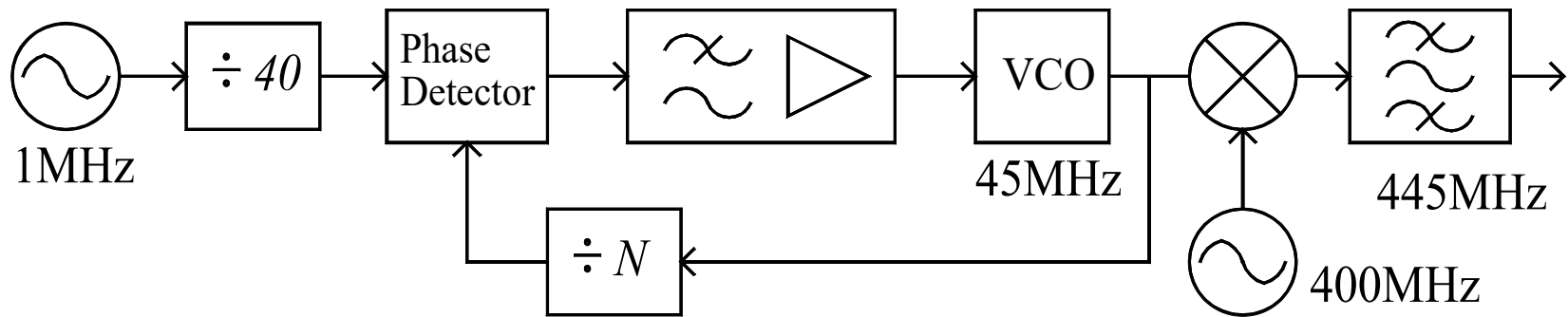
- Hard to build adjustable high-speed divider




## Alternatives

- Combine indirect and direct synthesis
  - PLL used to get range and step size, at low freq.
  - add fixed frequency to get required output
  - or run VCO at output frequency,
  - subtract fixed freq. before input to divider


# Double frequency with a d-type flip-flop

 

Draft1.asc

 

## Fractional- $N$ Divider

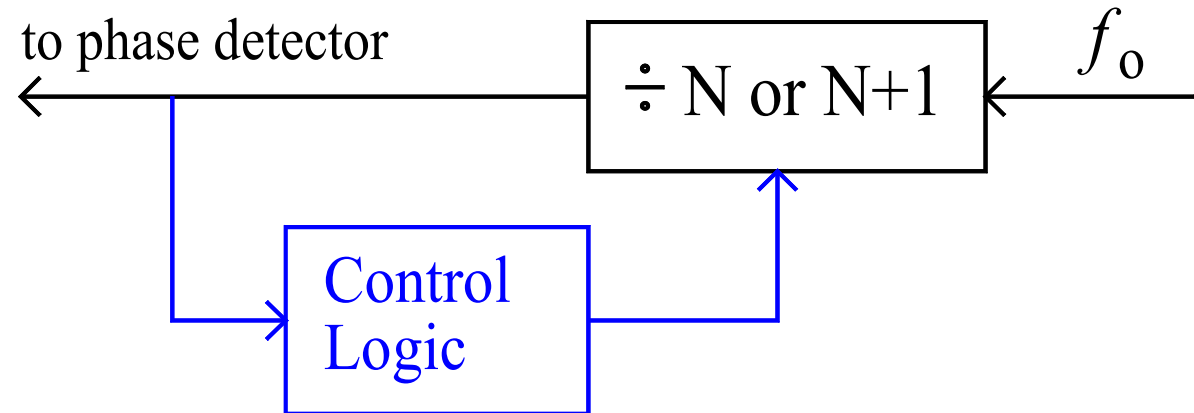


- Modified divider allows non-integer division
  - allows small step size with higher  $f_{ref}$
- High-speed divider, with 2 division ratios
  - *dual-modulus* divider
  - control logic counts output cycles:  
 $\div(N+1)$  for  $k$  cycles of each  $R$ , then  
 $\div N$  for  $R-k$  cycles of each  $R$

average division ratio = 
$$\frac{(N+1)k + N(R-k)}{R} = N + \frac{k}{R}$$



## Fractional- $N$ Synthesis

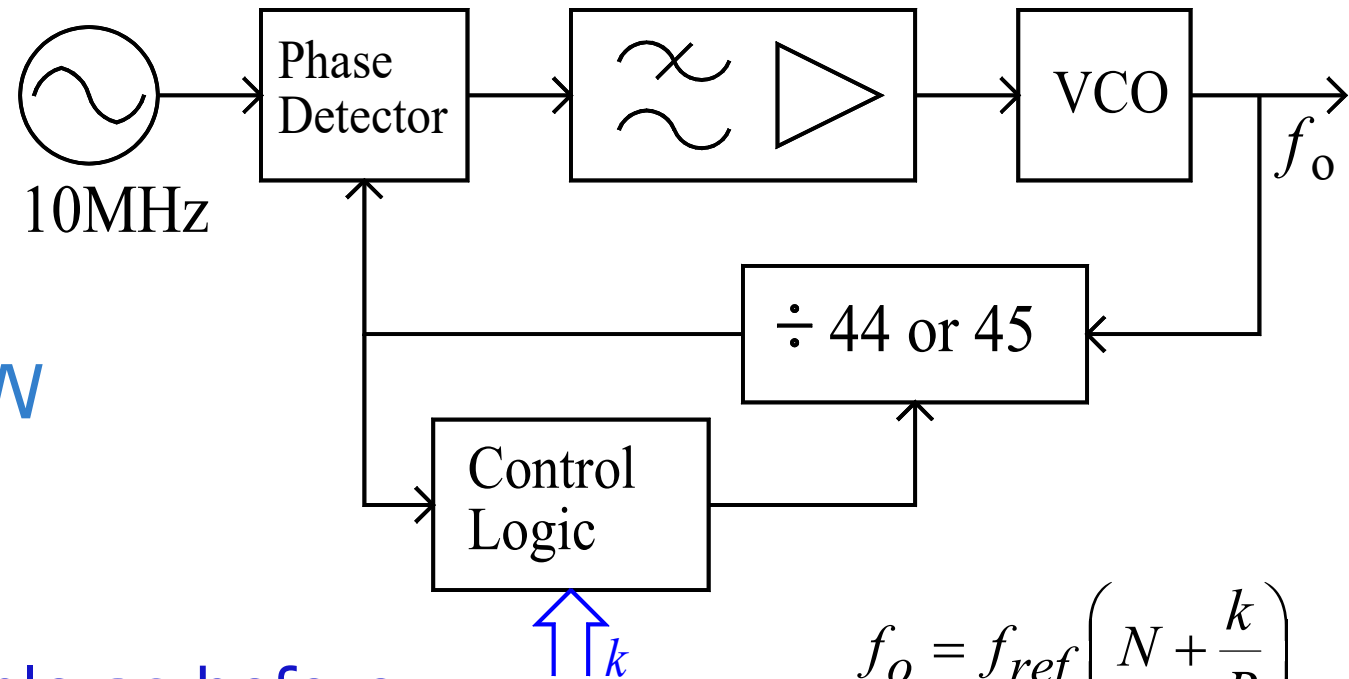

$$f_o = f_{ref} \left( N + \frac{k}{R} \right)$$

- Example as before

- want 440 to 450 MHz, 25 kHz steps
- now use  $f_{ref} = 10 \text{ MHz}$  (for example)
  - allows much larger loop filter BW
- Choose  $N$  to get frequency in required range
  - here  $N = 44$ , so minimum output freq. 44 times  $f_{ref}$
- choose  $R$  to get required step size ...
- adjust  $k$  to get specific frequency

$$f_o = 440 \text{ MHz} + k \times 25 \text{ kHz}$$




# Problems

- Spurious components in output
  - note periodic change in division ratio at  $\frac{f_{ref}}{R}$
  - $\Rightarrow$  periodic component in VCO control voltage
  - $\Rightarrow$  periodic frequency modulation of VCO
  - $\Rightarrow$  spurious components in output spectrum, at multiples of  $f_{ref}/R$  on both sides of  $f_o$ .
- Solutions:
  - randomise division adjustment
    - much more complex hardware...
  - add compensating signal to control voltage
    - since error is periodic and predictable...



# Direct Digital Synthesis

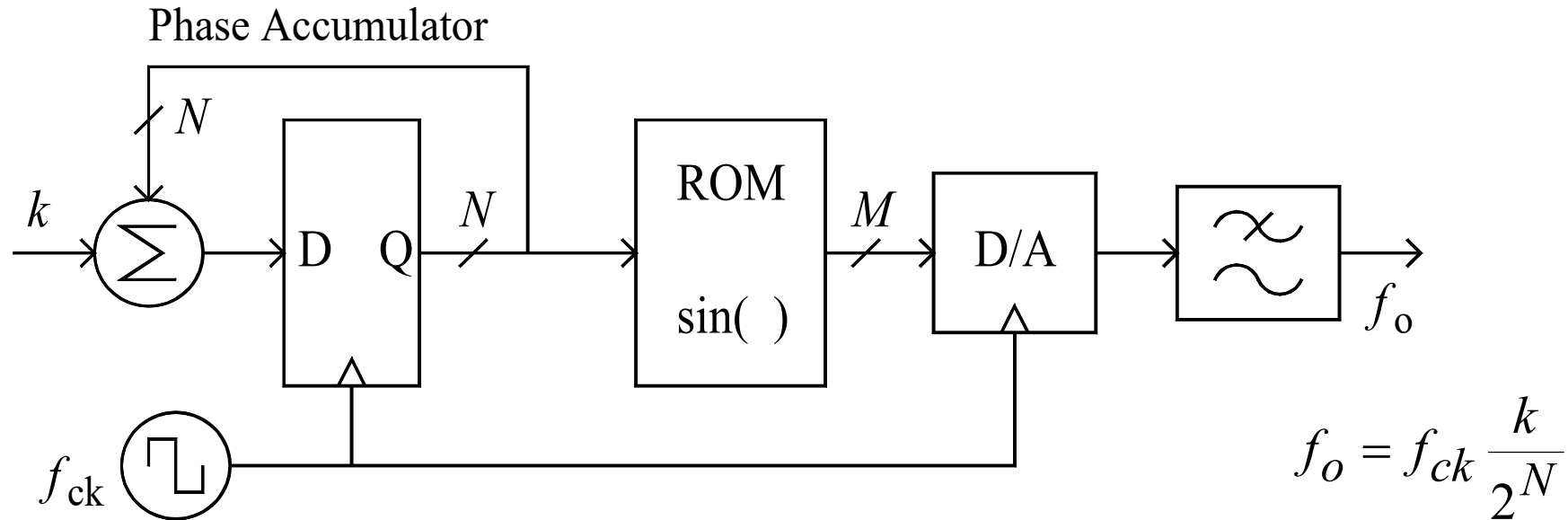


- Generate samples of signal digitally
  - add  $k$  to phase accumulator on each clock
  - so phase value advances at adjustable rate
  - overflows regularly - view as angle, 0 to  $2\pi$
  - ROM gives  $\sin( )$  of this phase angle
  - apply samples to D/A converter, reconstruct



## DDS

$$f_o = f_{ck} \frac{k}{2^N}$$

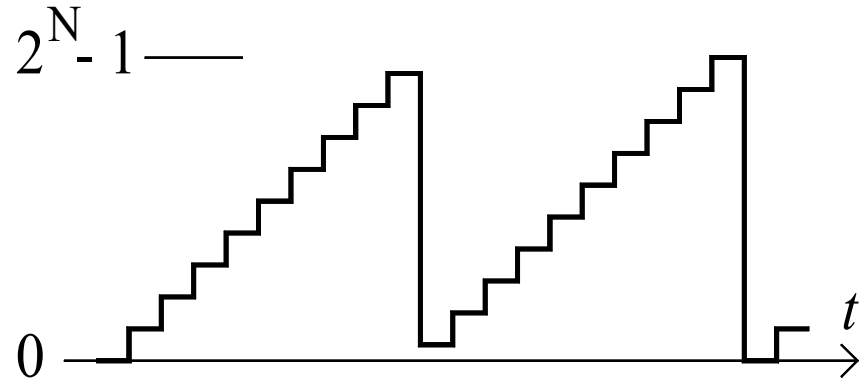


- For large  $N$ , extremely small frequency steps
  - low phase noise - due to clock jitter
- Many spurious outputs
  - phase has other periodic components
  - in example above, at half output frequency
  - quantisation errors - also periodic
- Output frequency
  - must be much less than clock frequency
  - also limited by speed of D/A converter
- Modulation possible - phase, frequency





## Example: AD9830

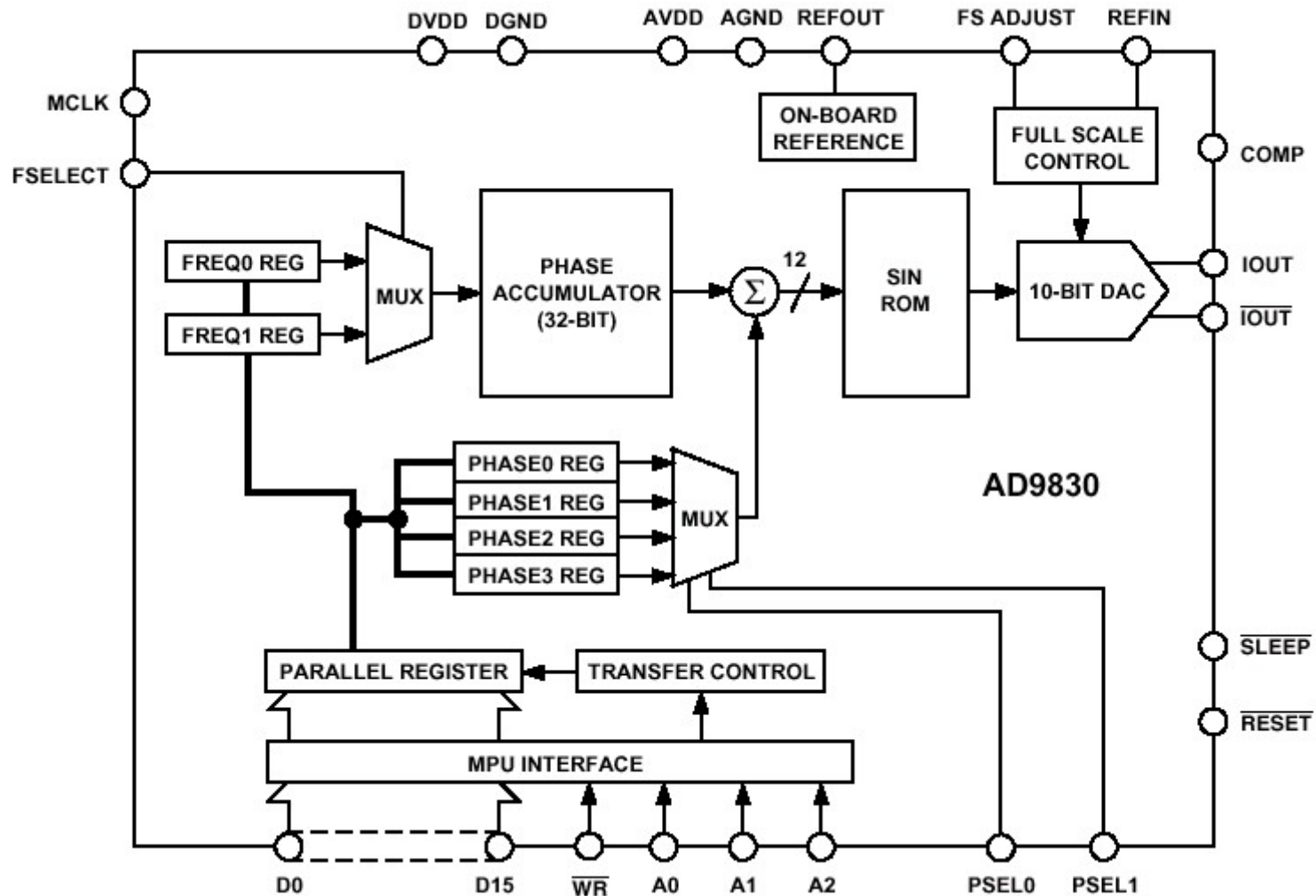

- 50 MHz max clock, 32-bit phase, 10-bit DAC
- 2 frequencies, 4 phase offsets stored

## Example: AD9910



- 1 GHz max clock
  - output up to 400 MHz (with good filter)
- 32-bit phase accumulator, 14-bit DAC
  - freq. resolution  $\sim 0.23$  Hz at 1 GHz clock.

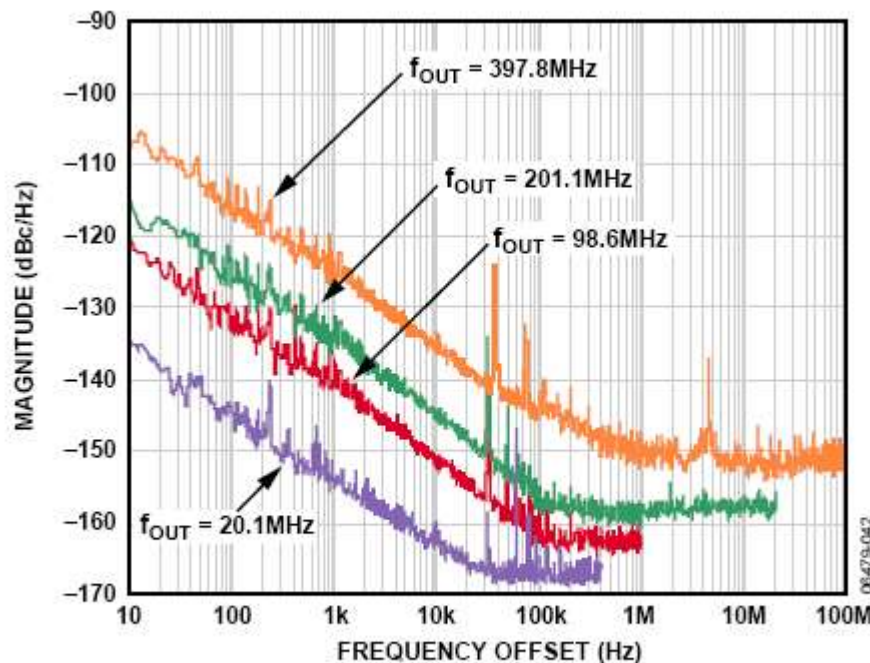


Figure 15. Residual Phase Noise Plot, 1 GHz Operation with PLL Disabled

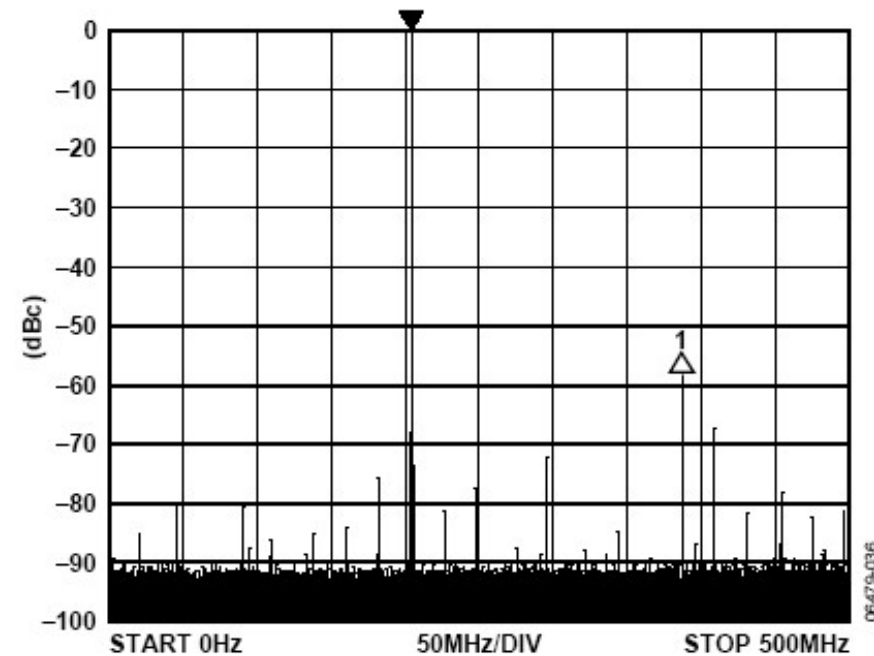


Figure 10. Wideband SFDR at 204 MHz, REFCLK = 1 GHz